

Fundamentals of Electrical and Electronics Engineering (FEEE)

SUB CODE: ECE1002

T-P-C: 3-2-4

Lecture-6

Faculty

Dr. Rajasekhar N V


Associate Professor G-1

SENSE, VIT-AP University


Mail: rajasekhar.venkata@vitap.ac.in

Cabin: Faculty Area 424-C:AB-1


Problem: Find all branch currents?

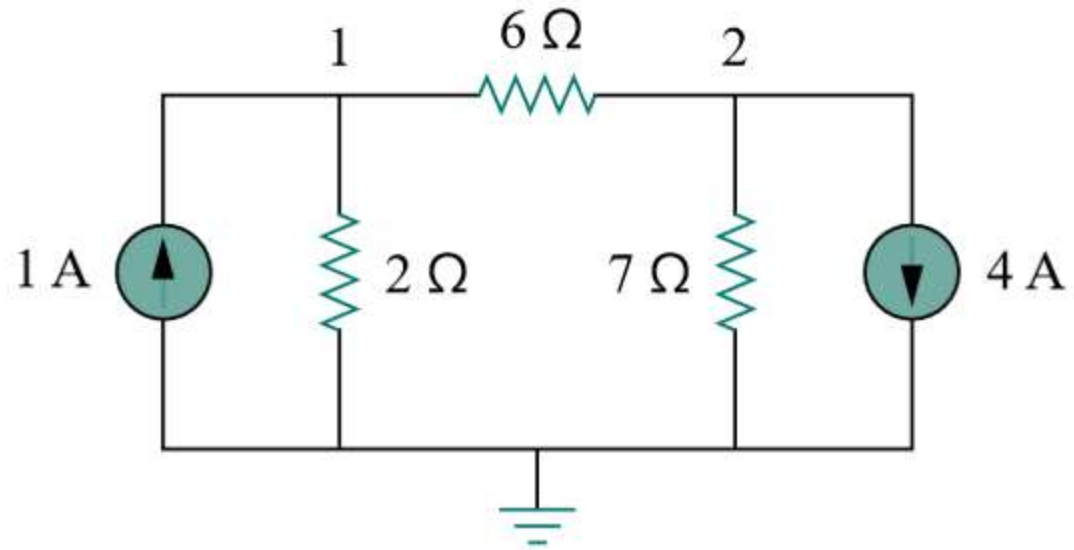


Problem: Find all branch currents?

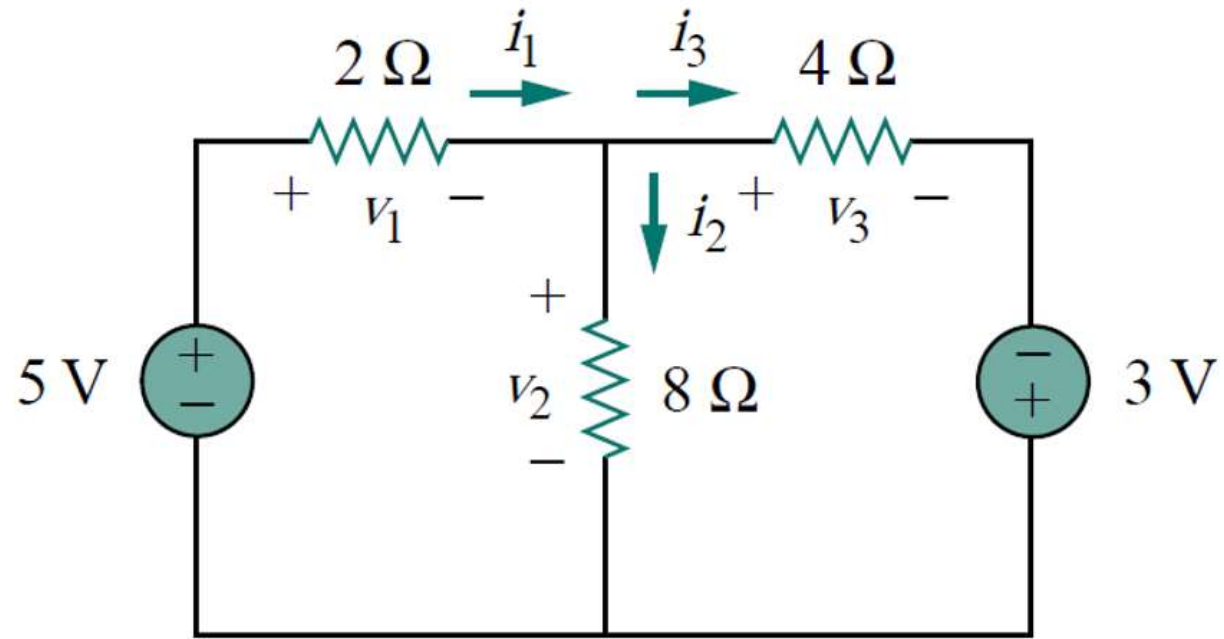

Problem: Find all branch currents?

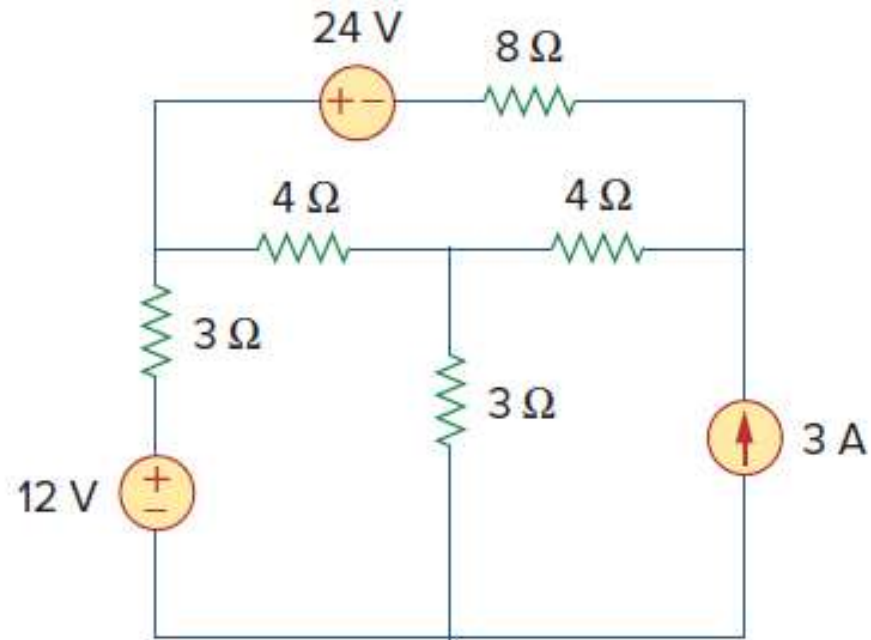


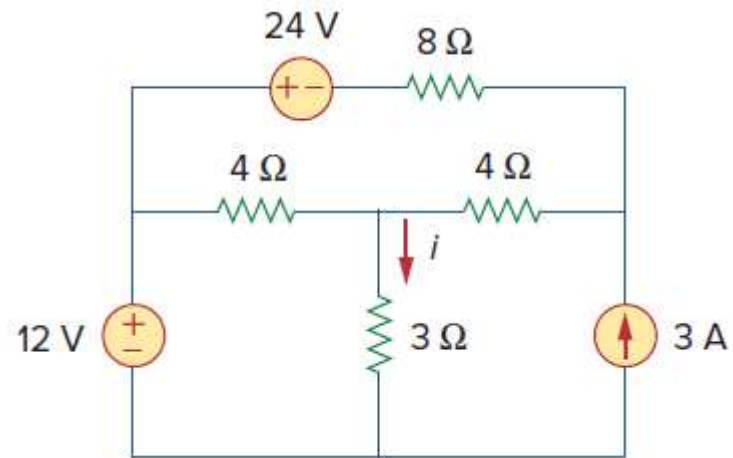Problem : Using the superposition theorem, find “i” in the circuit






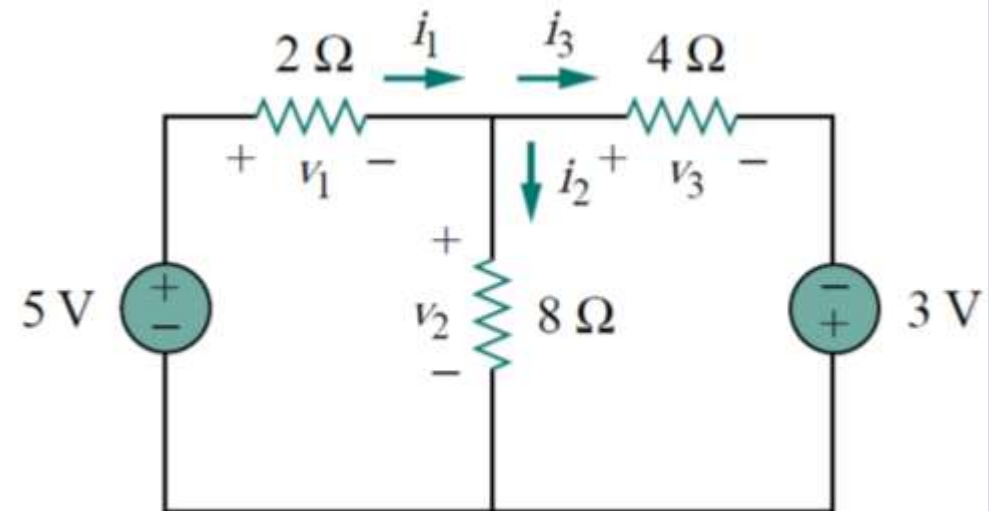2. Kirchhoff's Voltage Law (KVL)

- Kirchhoff's second law is based on the principle of conservation of energy.
- Kirchhoff's voltage law (KVL) states that the algebraic sum of all voltages around a closed path (or loop) is zero.
- Mathematically, KVL implies that $\sum V = 0$, *around a loop*.
- KVL can be applied in two ways: by taking either a clockwise or a counterclockwise trip around the loop. Either way, the algebraic sum of voltages around the loop is zero.
- The sign on each voltage is the polarity of the terminal encountered first as we travel around the loop.




Apply KVL

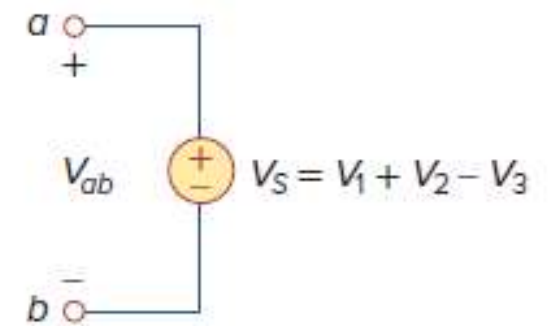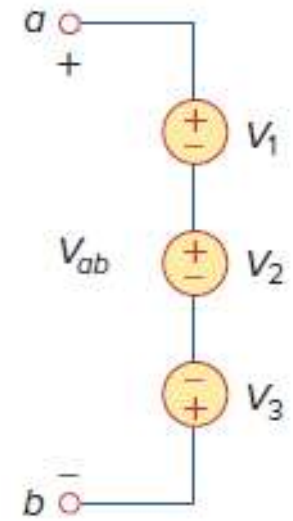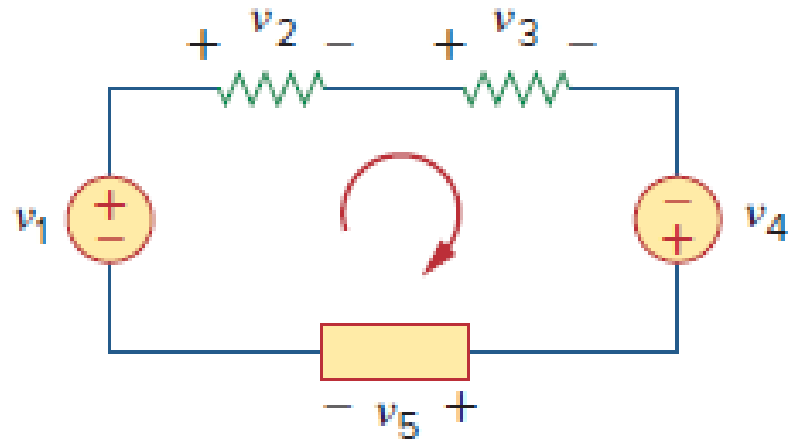


(b)

Problem-1: find v_1 and v_2

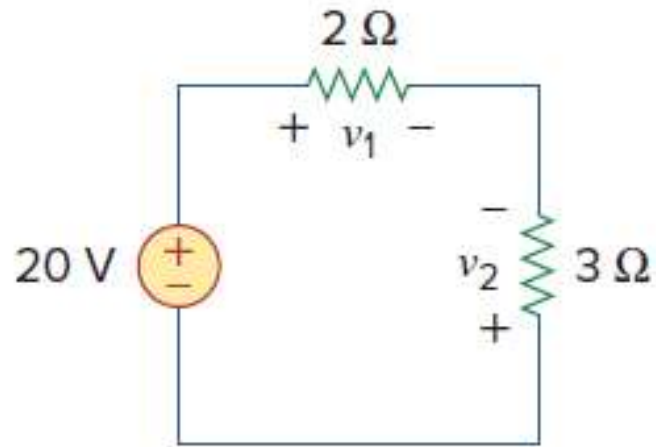

Problem-2: find v_1 and v_2

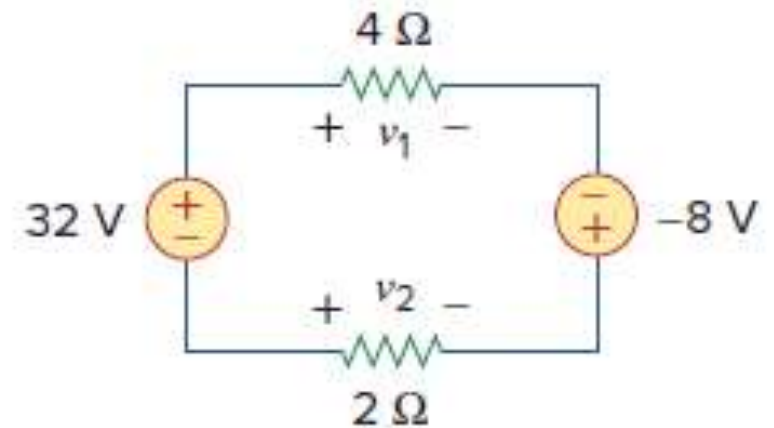

Series Resistors and Voltage Division

$$V = V_1 + V_2 \quad (KVL)$$

$$V_1 = i \times R_1 ; V_2 = i \times R_2 \quad (Ohms \text{ Law})$$


$$V = V_1 + V_2 = (i \times R_1) + (i \times R_2)$$

$$V = V_1 + V_2 = i \times (R_1 + R_2)$$

$$i = \frac{V}{(R_1 + R_2)}$$

$$V_1 = \frac{V}{(R_1 + R_2)} \times R_1$$
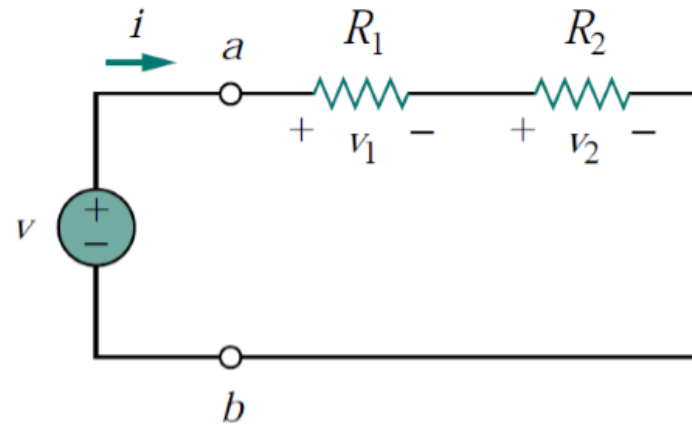
$$V_2 = \frac{V}{(R_1 + R_2)} \times R_2$$




Voltage across a resistor R_x in a series circuit with n resistors


$$V_x = \frac{V}{\sum_{i=1}^n R_i} \times R_x$$

Equivalent resistance of a series circuit with n resistors, R_{Eq}

$$R_{Eq} = \sum_{i=1}^n R_i$$

Problem:4

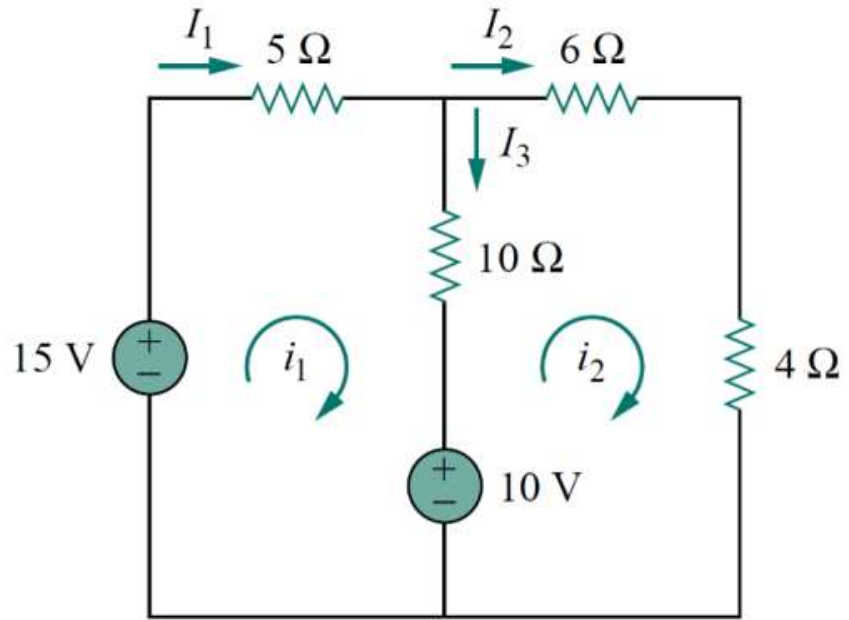

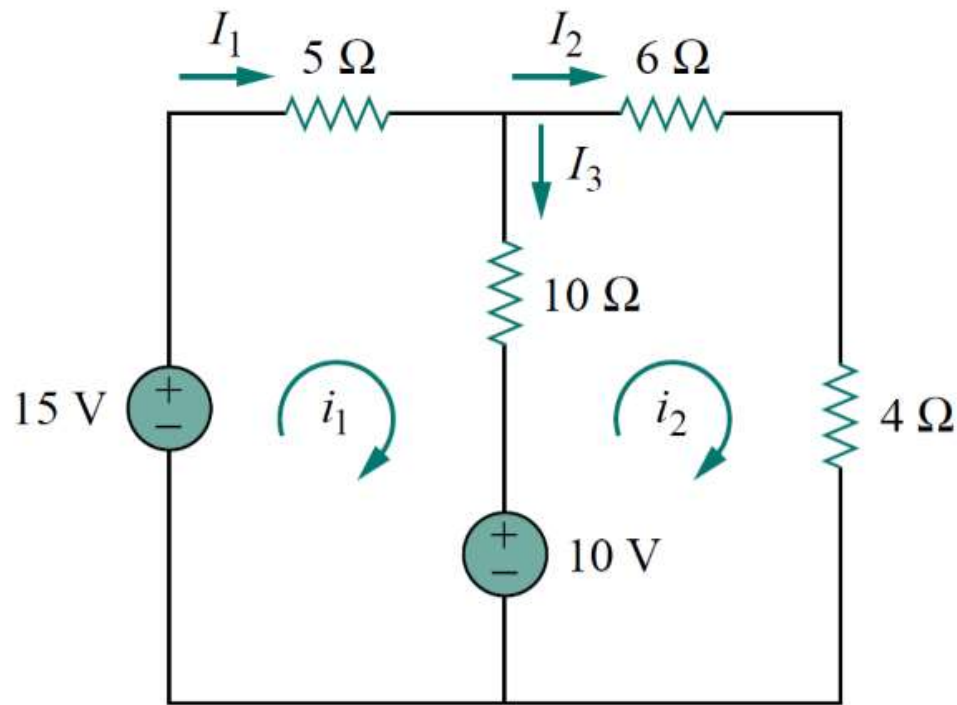

$$15i_1 - 10i_2 = 5 \quad (1)$$

$$-10i_1 + 20i_2 = 10 \quad (2)$$

$$i_1 = 1 \text{ A}; i_2 = 1 \text{ A}$$

$$I_1 = i_1 = 1 \text{ A}; I_2 = i_2 = 1 \text{ A}; I_3 = i_1 - i_2 = 0 \text{ A}$$

$$P_{5\Omega} = I_1^2 \times R = 1^2 \times 5 = 5W; P_{6\Omega} = I_2^2 \times R = 1^2 \times 6 = 6W; P_{10\Omega} = 0W;$$

Determine the power dissipated in all the resistors in the circuit using mesh current analysis.

There are two meshes 1 & 2.

The mesh currents are I_1 and I_2 .

At mesh 1:

$$5i_1 + 10(i_1 - i_2) + 10 - 15 = 0 \quad (1)$$

At mesh 2:

$$6i_2 + 4i_2 + -10 - 10(i_1 - i_2) = 0 \quad (2)$$

Problem:6

