

Fundamentals of Electrical and Electronics Engineering (FEEE)

SUB CODE: ECE1002

T-P-C: 3-2-4

Lecture-9

Faculty

Dr. Rajasekhar N V

Associate Professor G-1

SENSE, VIT-AP University

Mail: rajasekhar.venkata@vitap.ac.in

Cabin: Faculty Area 424-C:AB-1


Network Theorems


1. Superposition Theorem
2. Thevenin Theorem
3. Maximum Power Transfer Theorem

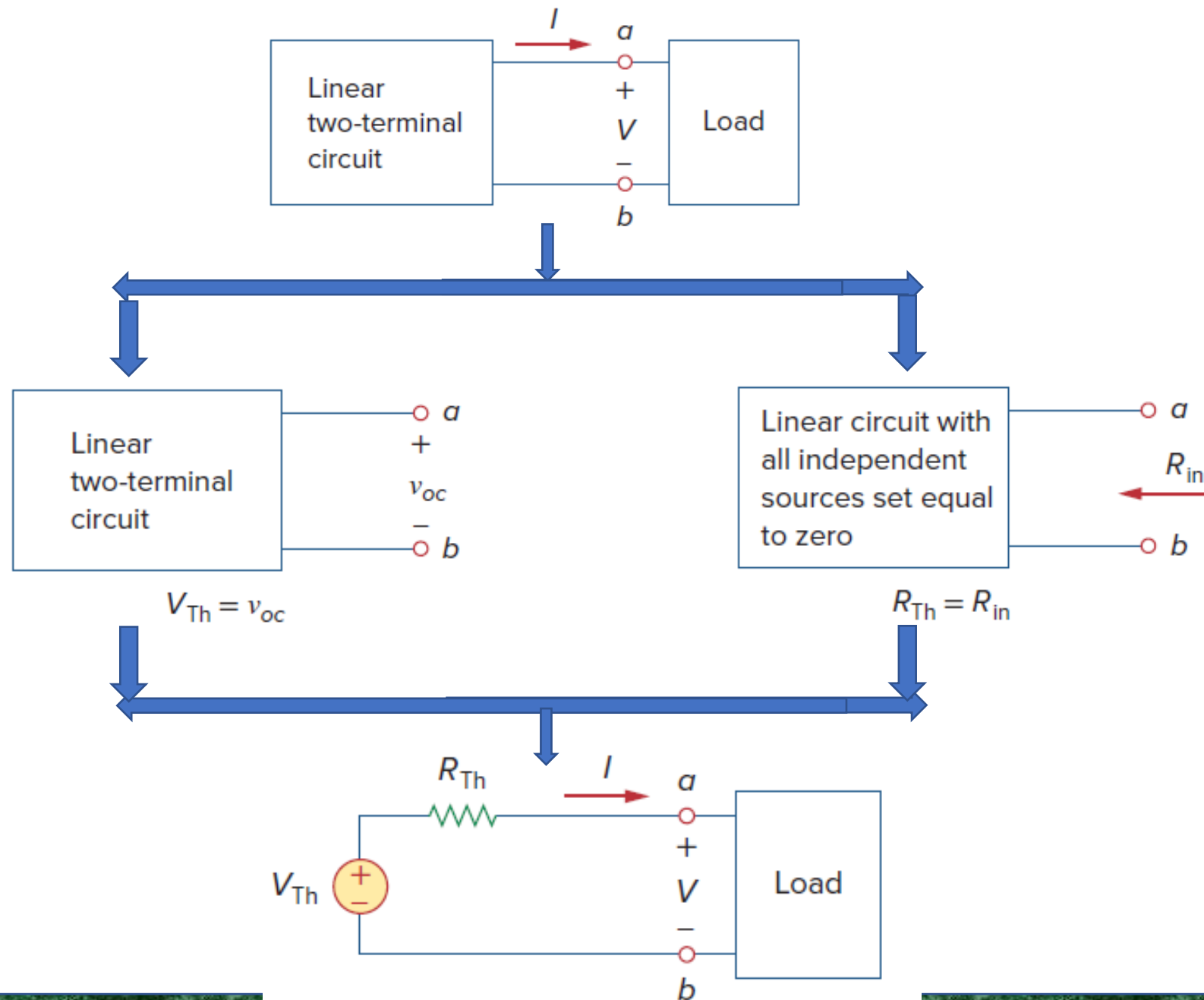2.Thevenin's Theorem

- Thevenin's theorem states that a linear two-terminal circuit can be replaced by an equivalent circuit consisting of a voltage source V_{Th} in series with a resistor R_{Th} .
- V_{Th} is the open-circuit voltage at the terminals and R_{Th} is the input or equivalent resistance at the terminals when the independent sources are turned off.






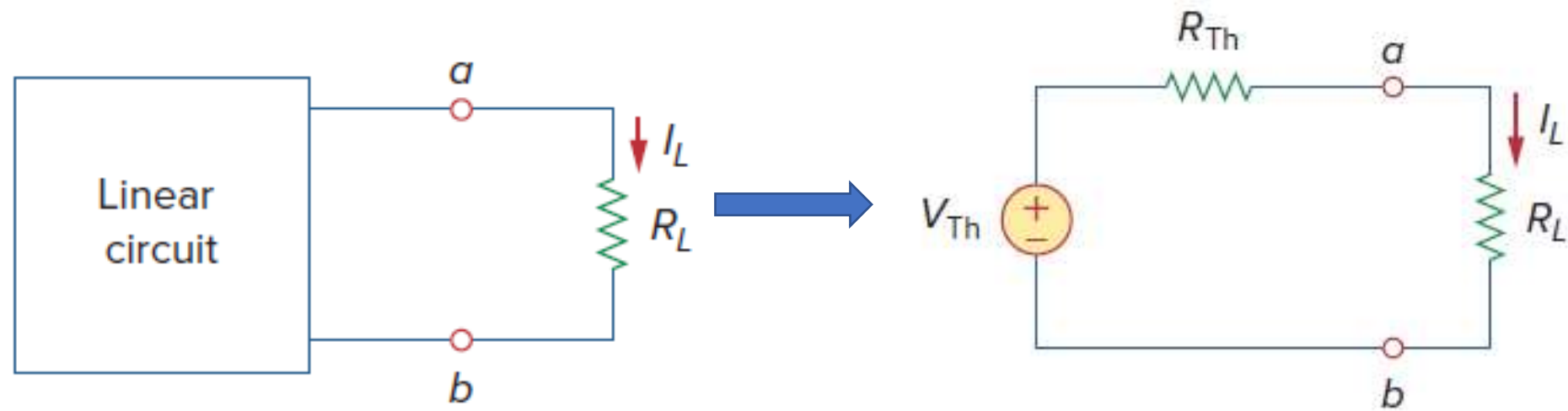


P-1

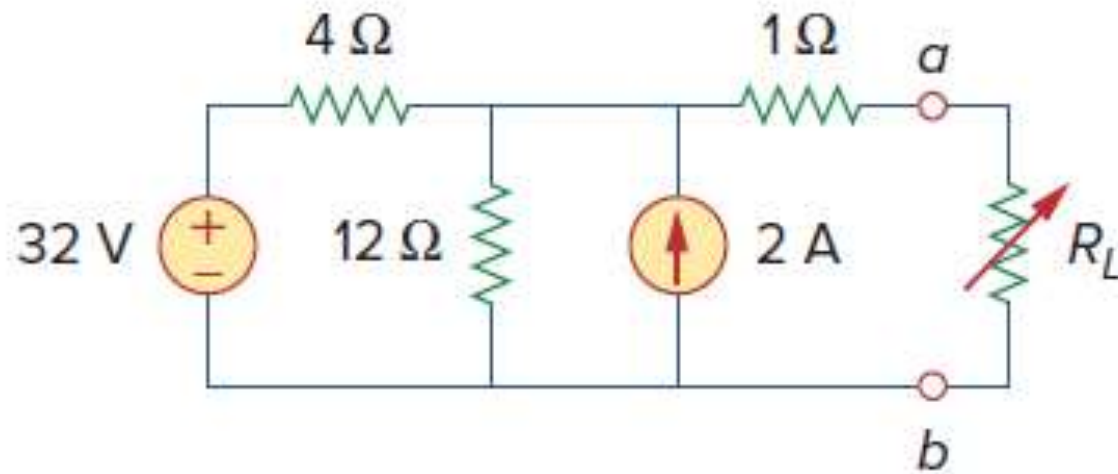
Find the Thevenin equivalent circuit of the circuit shown in Fig, to the left of the terminals a - b . Then find the current through $R_L = 10\ \Omega$, $15\ \Omega$, and $40\ \Omega$.



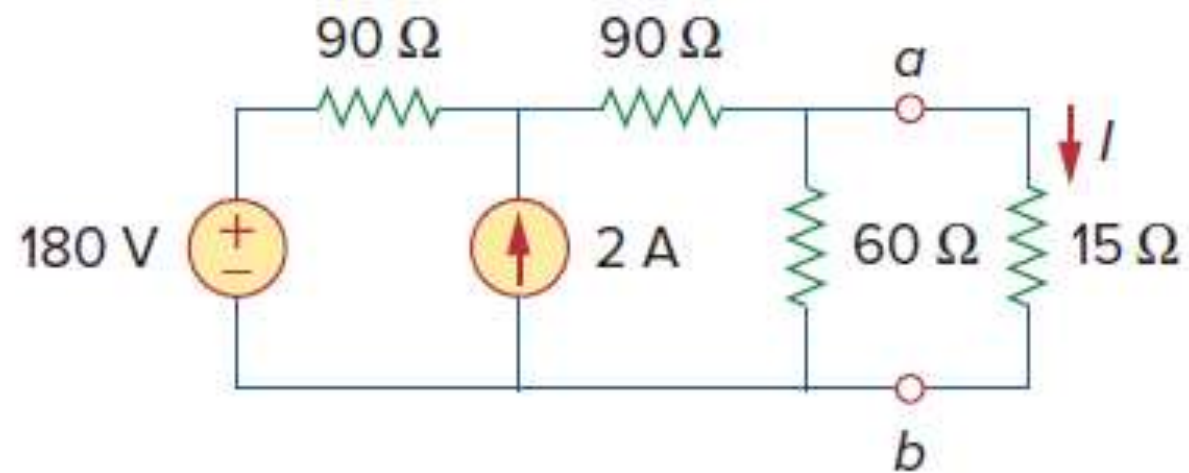
P-2: Find the Thevenin equivalent circuit of the circuit shown in Fig, to the left of the terminals a - b . Then find the current through $15\ \Omega$.



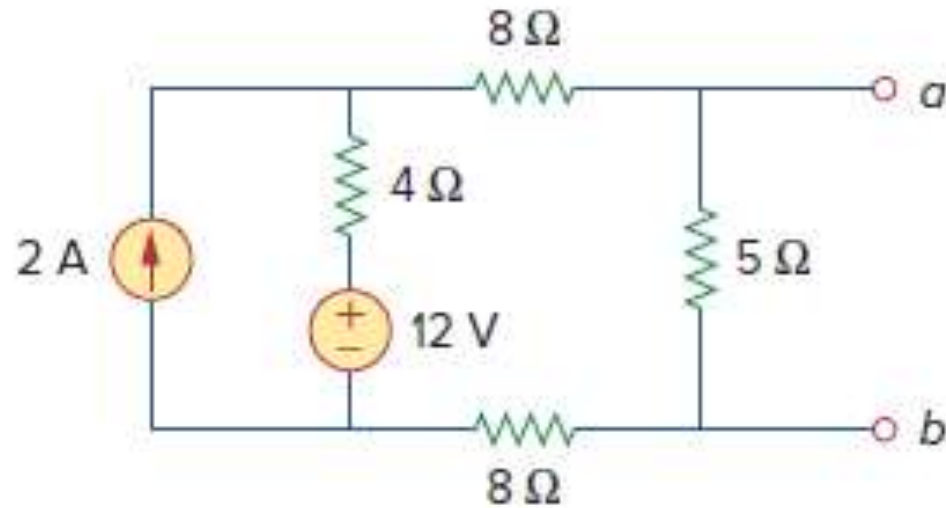
P-3: Find the Thevenin equivalent circuit of the circuit shown in Fig, to the left of the terminals a - b . Then find the current through if $R_L=10\ \Omega$ between a - b .




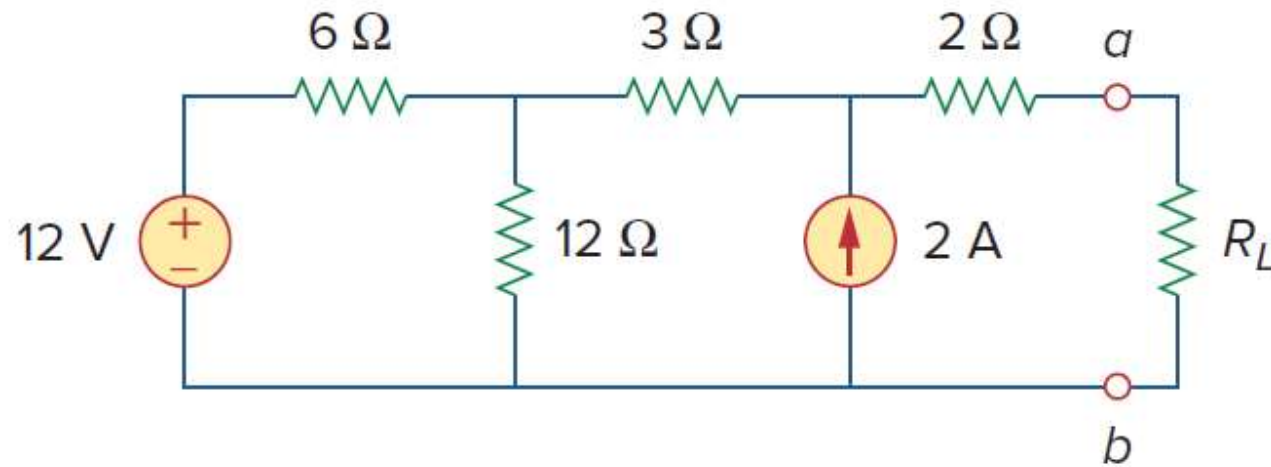P-4: Find the Thevenin equivalent circuit of the circuit shown in Fig, to the left of the terminals a - b . Then find the current through $R_L=10\ \Omega$.



III). Maximum Power Transfer Theorem

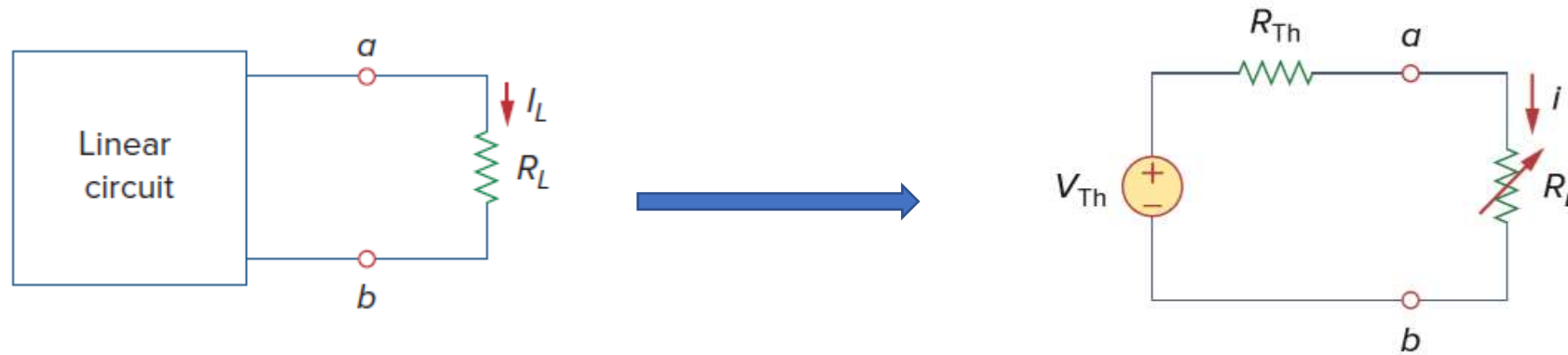

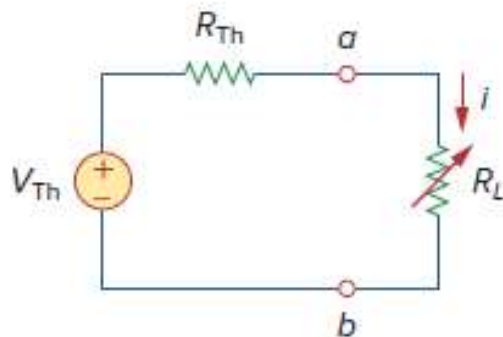

$$p = i^2 R_L = \left(\frac{V_{Th}}{R_{Th} + R_L} \right)^2 R_L$$

To prove the maximum power transfer theorem, we differentiate p with respect to R_L and set the result equal to zero. We obtain


$$\frac{dp}{dR_L} = V_{Th}^2 \left[\frac{(R_{Th} + R_L)^2 - 2R_L(R_{Th} + R_L)}{(R_{Th} + R_L)^4} \right]$$

$$= V_{Th}^2 \left[\frac{(R_{Th} + R_L - 2R_L)}{(R_{Th} + R_L)^3} \right] = 0$$

$$0 = (R_{Th} + R_L - 2R_L) = (R_{Th} - R_L)$$

The maximum power transferred to the load when

$$R_L = R_{Th}$$


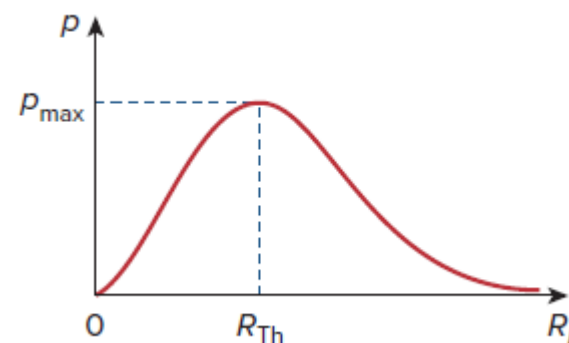


$$p = i^2 R_L = \left(\frac{V_{Th}}{R_{Th} + R_L} \right)^2 R_L$$

The maximum power transferred to the load is


$$p_{max} = \frac{V_{Th}^2}{4R_{Th}}$$

Maximum Power Transfer Theorem

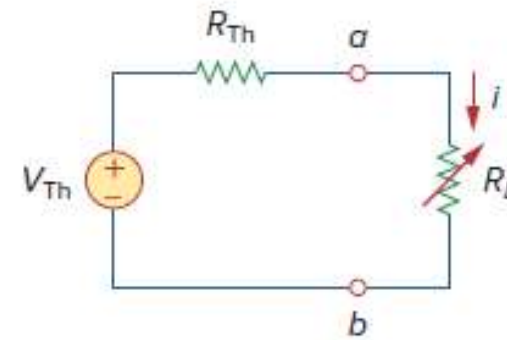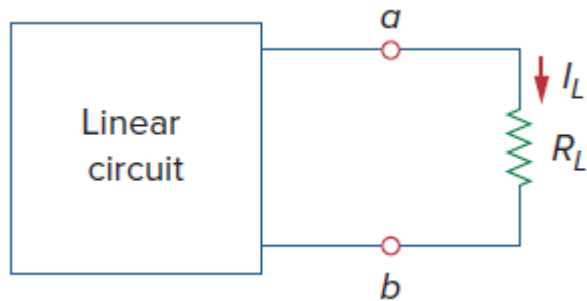


- Maximum Power transferred to the load when load resistance equal to source resistance.

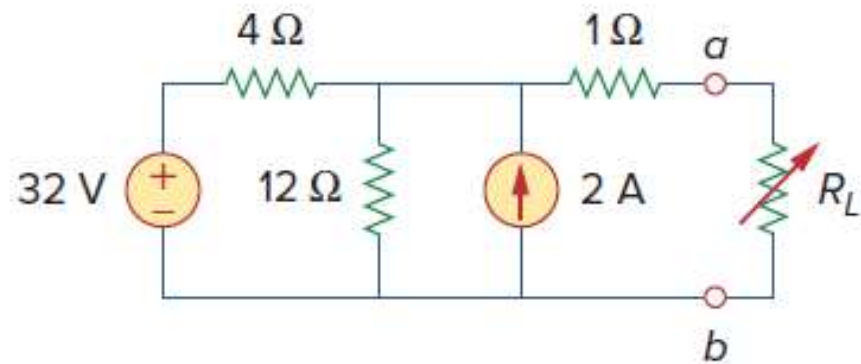Find the value of R_L for maximum power transfer in the circuit of Fig. Find the maximum power transferred to the load.



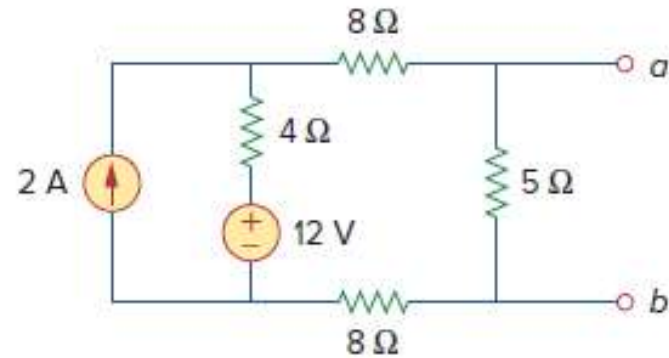Find the value of R_L for maximum power transfer in the circuit of Fig. Find the maximum power transferred to the load.



Find the value of R_L for maximum power transfer in the circuit of Fig. Find the maximum power transferred to the load.

