

Fundamentals of Electrical and Electronics Engineering (FEEE)

SUB CODE: ECE1002

T-P-C: 3-2-4

Lecture-11

Faculty

Dr. Rajasekhar N V

Associate Professor G-1


SENSE, VIT-AP University

Mail: rajasekhar.venkata@vitap.ac.in

Cabin: Faculty Area 424-C:AB-1

Assignment-2

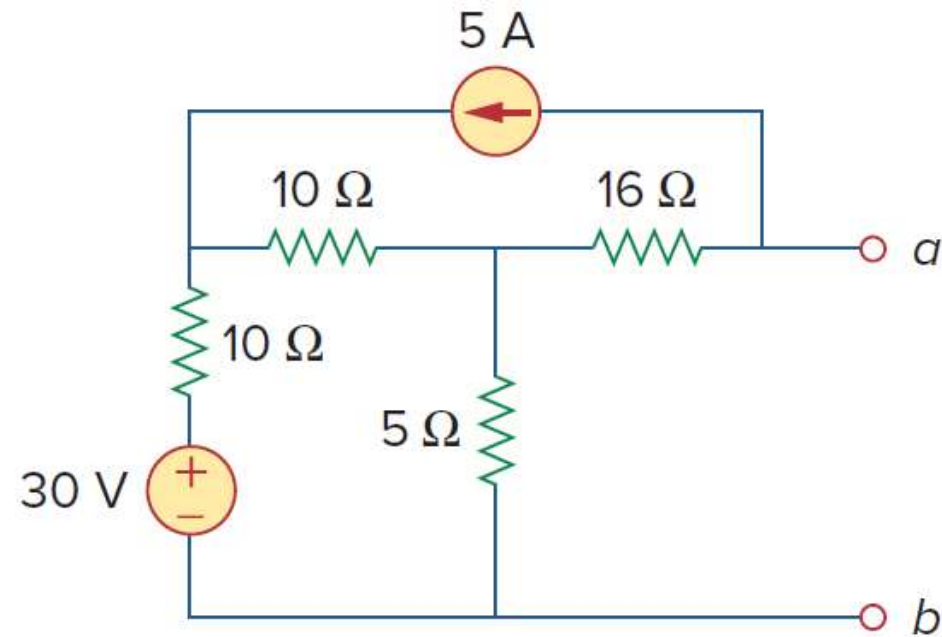1. Obtain the Thevenin equivalent at terminals a-b of the circuit shown in Fig.



2. Use superposition to obtain i_o in the circuit of Fig.

