

Fundamentals of Electrical and Electronics Engineering (FEEE)

SUB CODE: ECE1002

T-P-C: 3-2-4

Lecture-12

Faculty

Dr. Rajasekhar N V

Associate Professor G-1






SENSE, VIT-AP University

Mail: rajasekhar.venkata@vitap.ac.in


Cabin: Faculty Area 424-C:AB-1

Practice Problems

Find R_{eq}

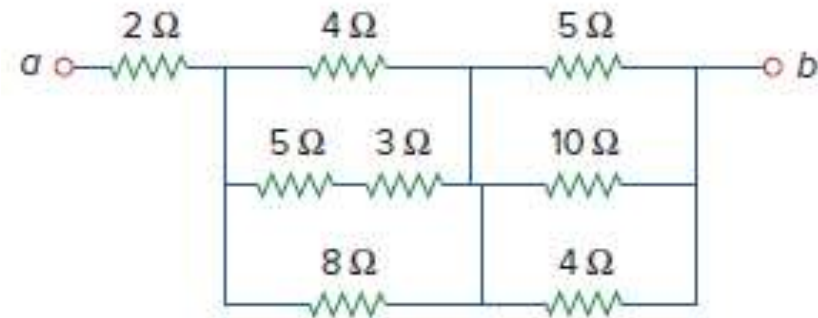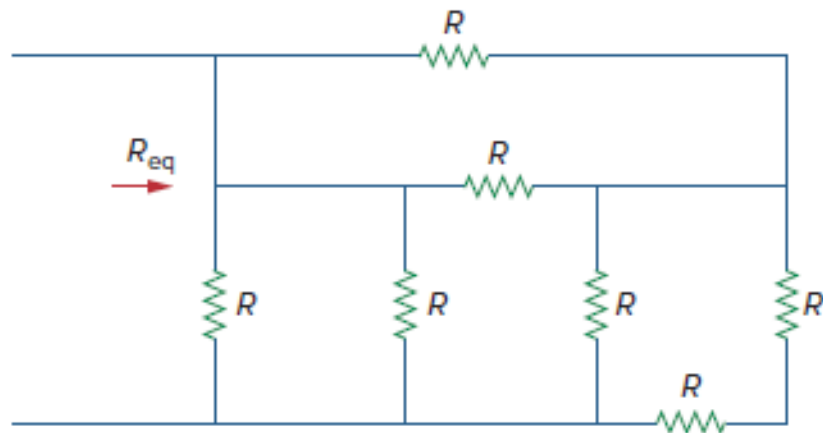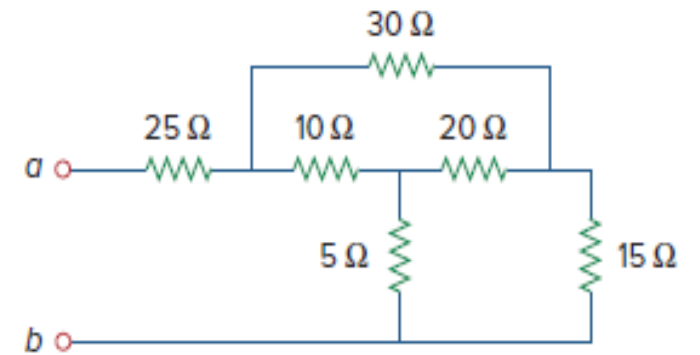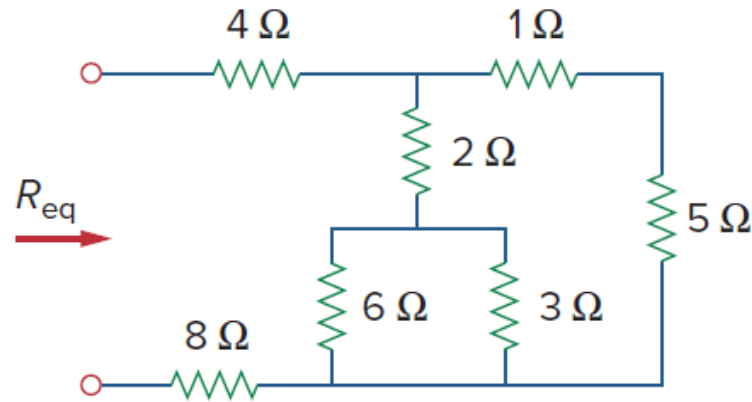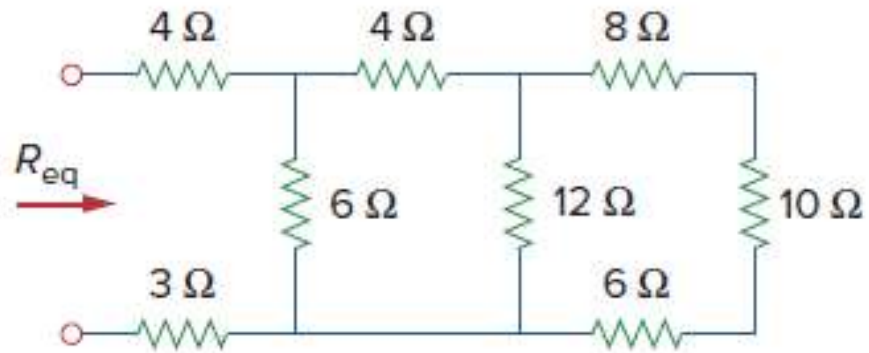

Find I and V in the circuit of Fig

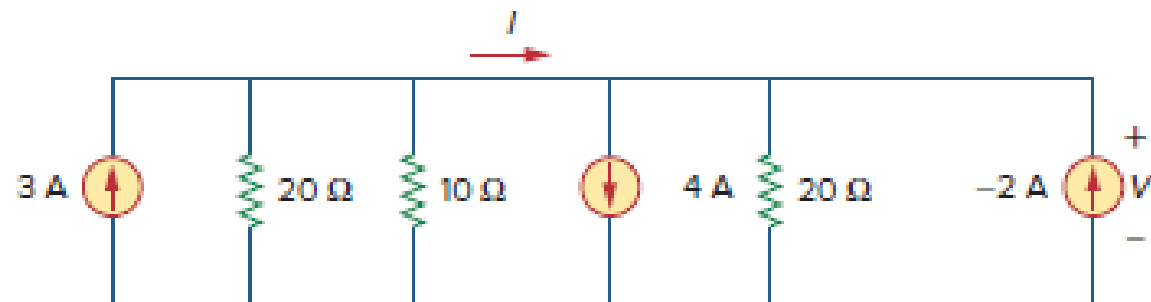

Apply the superposition principle to find v_o in the circuit of Fig

