

Fundamentals of Electrical and Electronics Engineering (FEEE)

SUB CODE: ECE1002

T-P-C: 3-2-4

Lecture-13

Faculty

Dr. Rajasekhar N V

Associate Professor G-1


SENSE, VIT-AP University

Mail: rajasekhar.venkata@vitap.ac.in


Cabin: Faculty Area 424-C:AB-1

Practice Problems

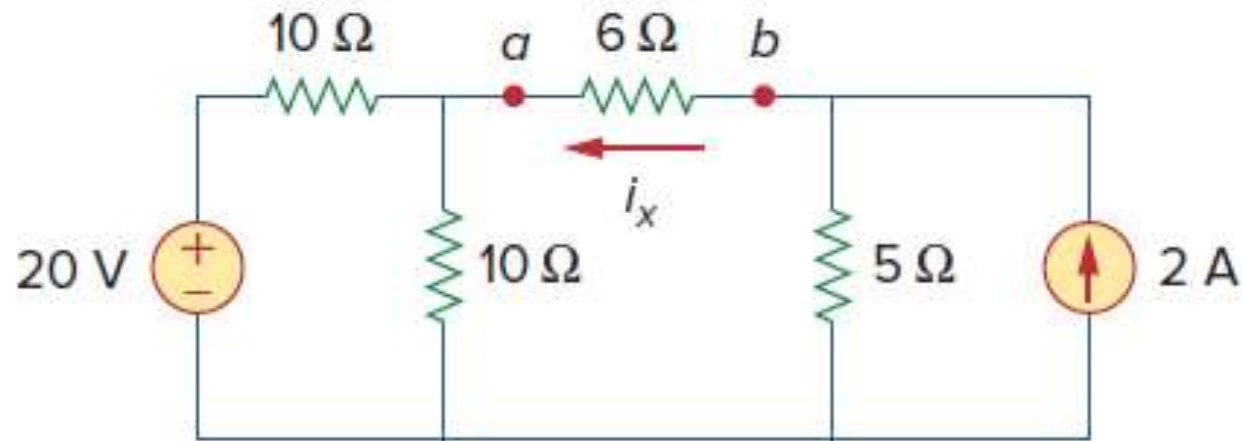
Find the Thevenin equivalent looking into terminals a-b of the circuit in Fig. and solve for i_x .



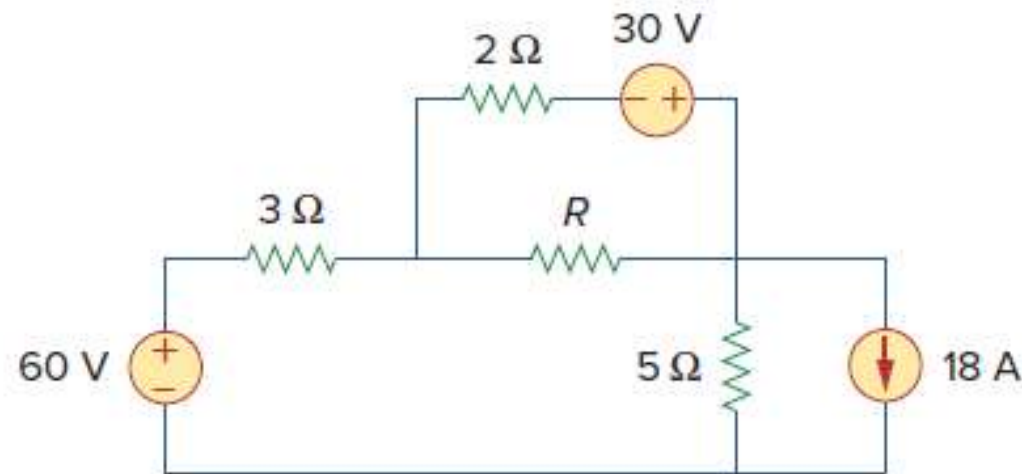
Find the maximum power that can be delivered to the resistor R in the circuit of Fig.



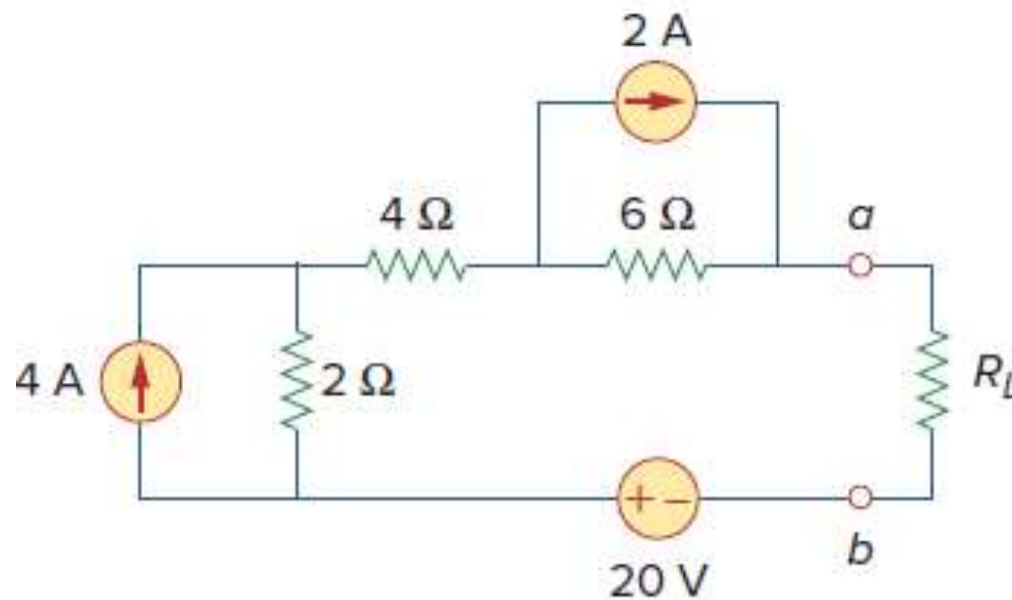- (a) For the circuit in Fig. , obtain the Thevenin equivalent at terminals $a-b$.
- (b) Calculate the current in $R_L = 13 \Omega$.
- (c) Find R_L for maximum power deliverable to R_L .
- (d) Determine that maximum power.



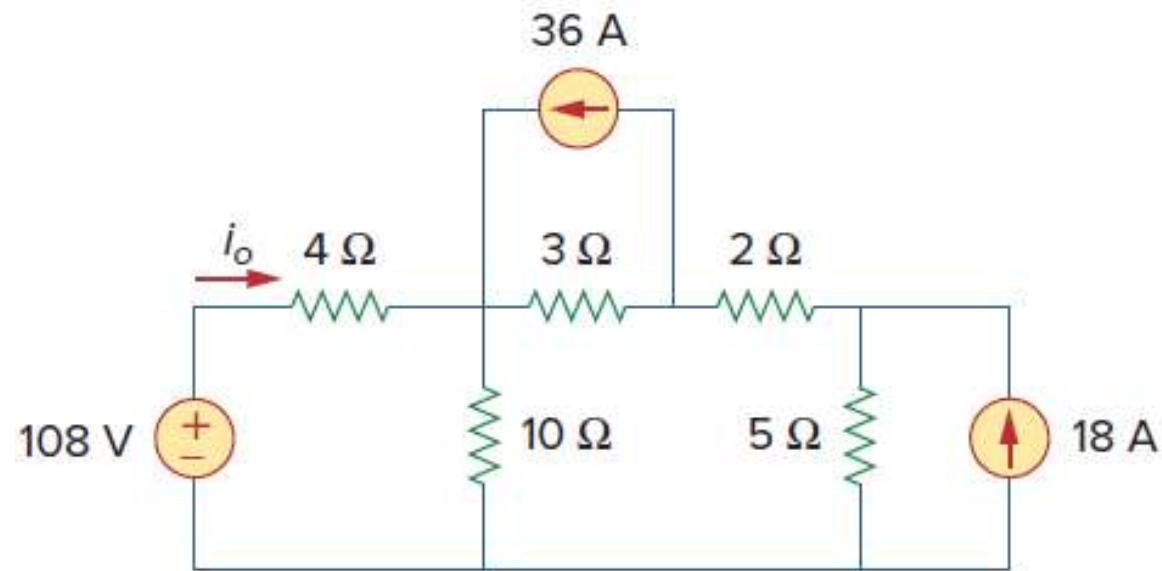1. Use superposition to obtain i_o in the circuit of Fig.



2. Obtain the Thevenin equivalent at terminals a-b of the circuit shown in Fig.

