

Fundamentals of Electrical and Electronics Engineering (FEEE)

SUB CODE: ECE1002

T-P-C: 3-2-4

Lecture-19

Faculty

Dr. Rajasekhar N V

Associate Professor G-1

SENSE, VIT-AP University

Mail: rajasekhar.venkata@vitap.ac.in

Cabin: Faculty Area 424-C:AB-1

VII. Kirchhoff's Laws in the Frequency Domain:

- We cannot do circuit analysis in the frequency domain without Kirchhoff's current and voltage laws. Therefore, we need to express them in the frequency domain.
- For KVL, let $v_1, v_2, \dots, v_n$ be the voltages around a closed loop. Then

$$v_1 + v_2 + \dots + v_n = 0$$



$$V_{m1} \cos(\omega t + \vartheta_1) + V_{m2} \cos(\omega t + \vartheta_2) + \dots + V_{mn} \cos(\omega t + \vartheta_n) = 0$$

$$\mathbf{V}_1 + \mathbf{V}_2 + \dots + \mathbf{V}_n = 0$$


[indicating that Kirchhoff's voltage law holds for phasors.]

- If $\mathbf{I}_1, \mathbf{I}_2, \dots, \mathbf{I}_n$ are the phasor forms of the sinusoids $i_1, i_2, \dots, i_n$, then
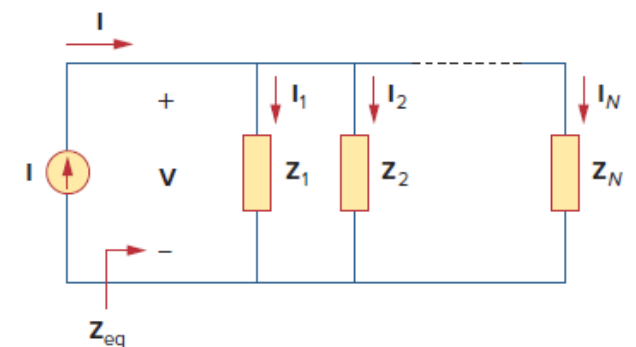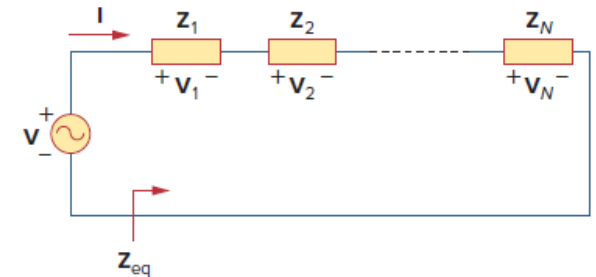
$$\mathbf{I}_1 + \mathbf{I}_2 + \dots + \mathbf{I}_n = 0$$




Impedance Combinations

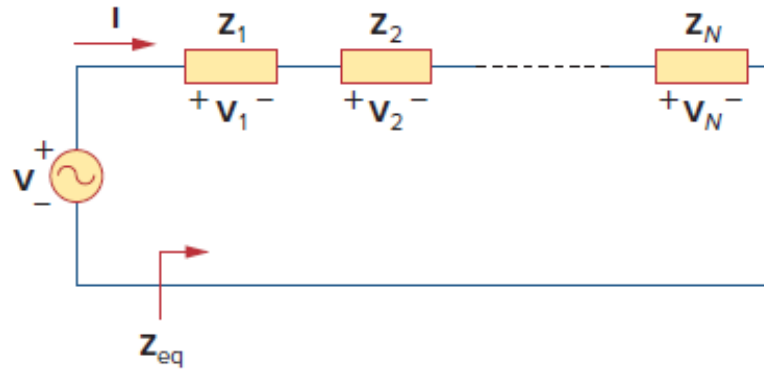

$$V = V_1 + V_2 + \dots + V_N = I(Z_1 + Z_2 + \dots + Z_N)$$

$$Z_{eq} = \frac{V}{I} = Z_1 + Z_2 + \dots + Z_N$$


$$Z_{eq} = Z_1 + Z_2 + \dots + Z_N$$

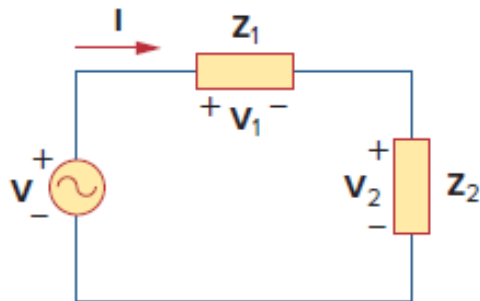

$$I = \frac{V}{Z_1 + Z_2}$$

$V_1 = Z_1 I$ and $V_2 = Z_2 I$, then
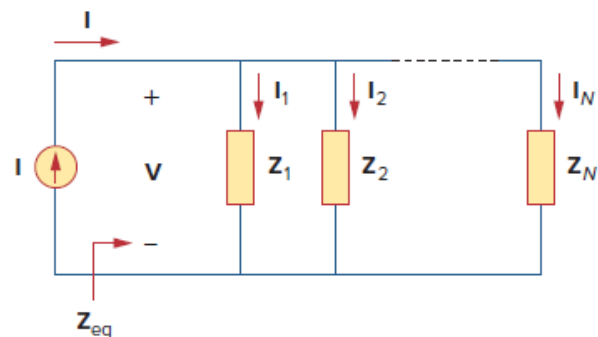
$$V_1 = \frac{Z_1}{Z_1 + Z_2} V, \quad V_2 = \frac{Z_2}{Z_1 + Z_2} V$$




$$I = I_1 + I_2 + \dots + I_N = V \left(\frac{1}{Z_1} + \frac{1}{Z_2} + \dots + \frac{1}{Z_N} \right)$$

$$\frac{1}{Z_{eq}} = \frac{I}{V} = \frac{1}{Z_1} + \frac{1}{Z_2} + \dots + \frac{1}{Z_N}$$

the equivalent admittance is

$$Y_{eq} = Y_1 + Y_2 + \dots + Y_N$$

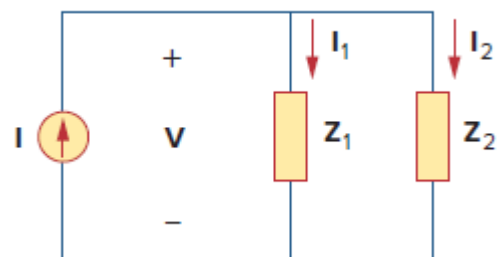

$$Z_{eq} = \frac{1}{Y_{eq}} = \frac{1}{Y_1 + Y_2} = \frac{1}{1/Z_1 + 1/Z_2} = \frac{Z_1 Z_2}{Z_1 + Z_2}$$

$$V = I Z_{eq} = I_1 Z_1 = I_2 Z_2$$

the currents in the impedances are

$$I_1 = \frac{Z_2}{Z_1 + Z_2} I, \quad I_2 = \frac{Z_1}{Z_1 + Z_2} I$$

1. The voltage $v = 12\cos(60t + 45^\circ)$ is applied to a 0.1-H inductor. Find the steady-state current through the inductor.

For the inductor, $\mathbf{V} = j\omega L\mathbf{I}$, where $\omega = 60$ rad/s

$$\mathbf{V} = 12 \angle 45^\circ \text{ V.}$$

$$\mathbf{I} = \frac{\mathbf{V}}{j\omega L}$$

$$= \frac{12 \angle 45^\circ}{j60 \times 0.1} = \frac{12 \angle 45^\circ}{6 \angle 90^\circ} = 2 \angle -45^\circ \text{ A}$$

Converting this to the time domain,

$$i(t) = 2 \cos(60t - 45^\circ) \text{ A}$$

2. If voltage $v = 25 \sin(100t - 15^\circ)$ V is applied to a $50 \mu\text{F}$ capacitor, calculate the current through the capacitor.

$$\mathbf{I} = j\omega C \mathbf{V} \quad \Rightarrow \quad \mathbf{V} = \frac{\mathbf{I}}{j\omega C}$$

3. Find $v(t)$ and $i(t)$ in the circuit shown in Fig.

From the voltage source $10 \cos 4t$, $\omega = 4$,

$$\mathbf{V}_s = 10 \angle 0^\circ \text{ V}$$

The impedance is


$$\mathbf{Z} = 5 + \frac{1}{j\omega C} = 5 + \frac{1}{j4 \times 0.1} = 5 - j2.5 \, \Omega$$

Hence the current

$$\begin{aligned} \mathbf{I} &= \frac{\mathbf{V}_s}{\mathbf{Z}} = \frac{10 \angle 0^\circ}{5 - j2.5} = \frac{10(5 + j2.5)}{5^2 + 2.5^2} \\ &= 1.6 + j0.8 = 1.789 \angle 26.57^\circ \text{ A} \end{aligned}$$

The voltage across the capacitor is
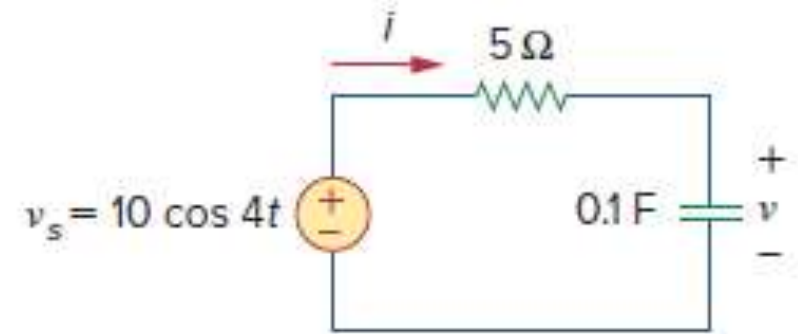
$$\begin{aligned} \mathbf{V} &= \mathbf{I} \mathbf{Z}_C = \frac{\mathbf{I}}{j\omega C} = \frac{1.789 \angle 26.57^\circ}{j4 \times 0.1} \\ &= \frac{1.789 \angle 26.57^\circ}{0.4 \angle 90^\circ} = 4.47 \angle -63.43^\circ \text{ V} \end{aligned}$$



$$i(t) = 1.789 \cos(4t + 26.57^\circ) \text{ A}$$

$$v(t) = 4.47 \cos(4t - 63.43^\circ) \text{ V}$$

Notice that $i(t)$ leads $v(t)$ by 90° as expected.

4. Determine $v(t)$ and $i(t)$.

$$I = \frac{V_s}{Z}$$


$$X_L = 10 \times 0.2 = 2 \Omega$$

$$Z = 4 + j2 \Omega$$

$$I = \frac{V_s}{Z} = \frac{5 \angle 0^\circ}{4 + j2} = 1.118 \angle 26.57^\circ \text{ A}$$

$$V = (1.118 \angle 26.57^\circ) \times (j2)$$

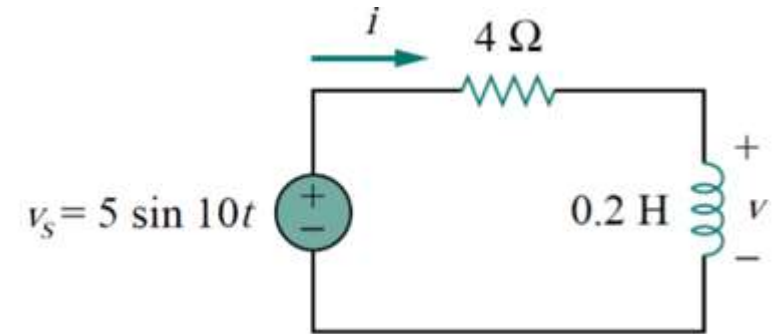
$$V = 2.236 \angle -63.43^\circ \text{ V}$$



$$i(t) = 1.118 \cos(10t + 26.57^\circ) \text{ A}$$


$$v(t) = 2.236 \cos(10t - 63.43^\circ) \text{ V}$$

5. Determine $v(t)$ and $i(t)$.

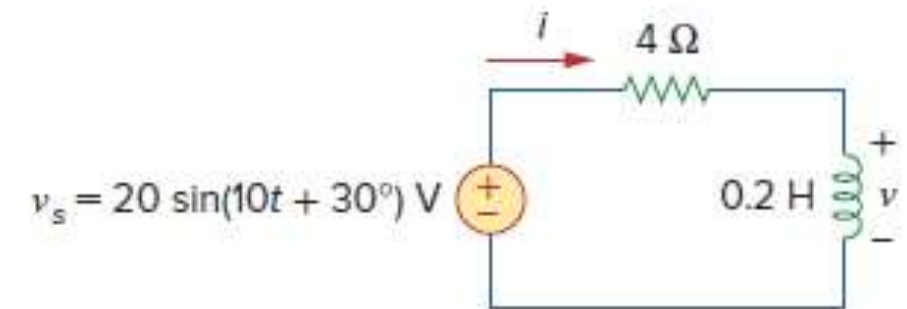

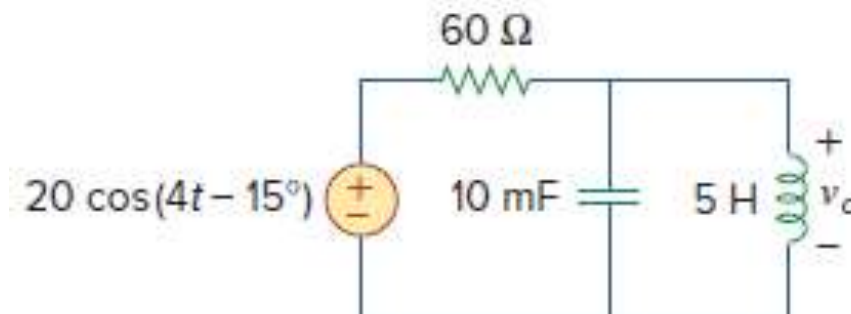6. Determine $v_o(t)$ in the circuit of Fig. below


- To do the analysis in the frequency domain, we must first transform the time domain circuit into the phasor domain equivalent.



$$v_s = 20 \cos(4t - 15^\circ) \Rightarrow \mathbf{V}_s = 20 \angle -15^\circ \text{ V},$$

$$\begin{aligned} 10 \text{ mF} &\Rightarrow \frac{1}{j\omega C} = \frac{1}{j4 \times 10 \times 10^{-3}} \\ \omega = 4 & \\ &= -j25 \Omega \end{aligned}$$
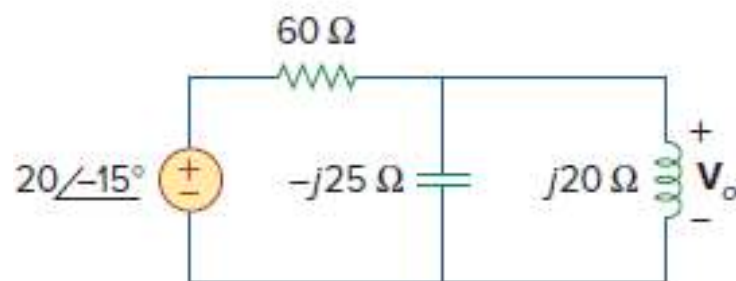
$$5 \text{ H} \Rightarrow j\omega L = j4 \times 5 = j20 \Omega$$



Z_1 = Impedance of the 60-Ω resistor


Z_2 = Impedance of the parallel combination of the 10-mF capacitor and the 5-H inductor

$$Z_1 = 60 \Omega \quad Z_2 = -j25 \parallel j20 = \frac{-j25 \times j20}{-j25 + j20} = j100 \Omega$$


$$\begin{aligned} \mathbf{V}_o &= \frac{Z_2}{Z_1 + Z_2} \mathbf{V}_s = \frac{j100}{60 + j100} (20 \angle -15^\circ) = (0.8575 \angle 30.96^\circ) (20 \angle -15^\circ) \\ &= 17.15 \angle 15.96^\circ \text{ V} \end{aligned}$$

$$v_o(t) = 17.15 \cos(4t + 15.96^\circ) \text{ V}$$

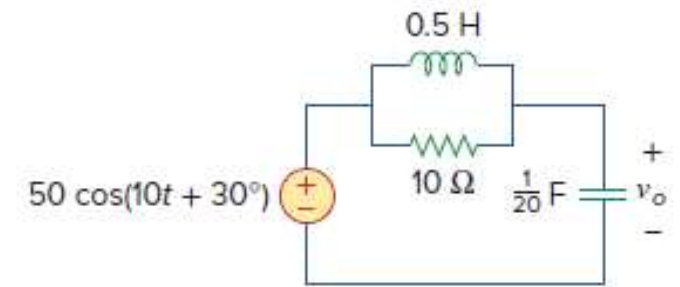
7. Determine $v_o(t)$ in the circuit of Fig. below



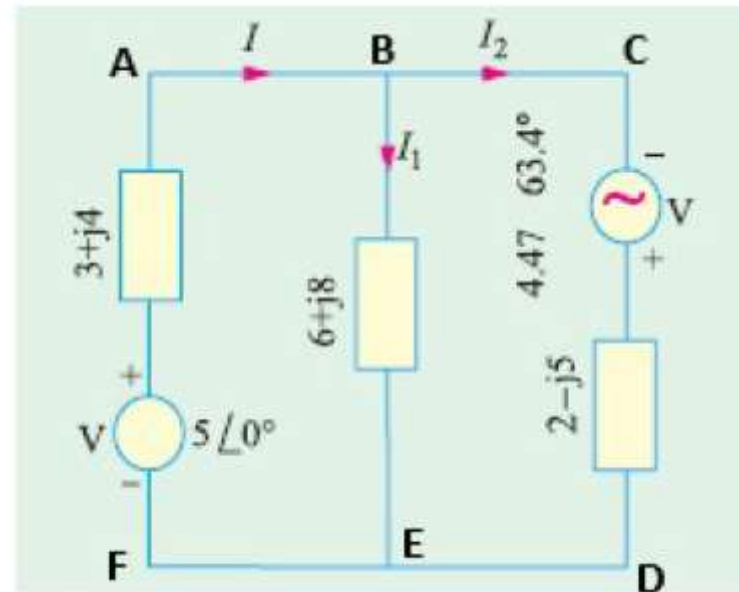8) Using Kirchhoff's Laws, calculate the current flowing through each branch of the circuit shown in figure below.



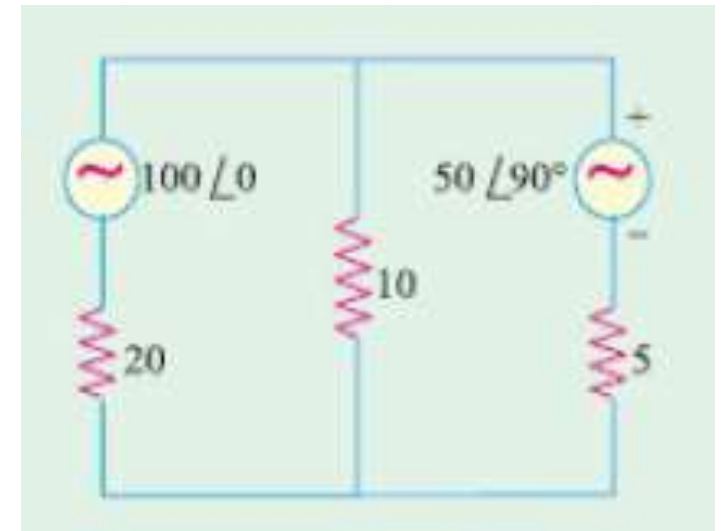2) Use Kirchhoff's laws to find the current flowing in each branch of the network shown in figure below.



9. Find current I in the circuit of Fig.

