



VIT-AP
UNIVERSITY

Fundamentals of Electrical and Electronics Engineering (FEEE)

SUB CODE: ECE1002

T-P-C: 3-2-4

Lecture-25

Faculty

Dr. Rajasekhar N V

Associate Professor G-1


SENSE, VIT-AP University

Mail: rajasekhar.venkata@vitap.ac.in

Cabin: Faculty Area 424-C:AB-1

Diode Equivalent:

Silicon:

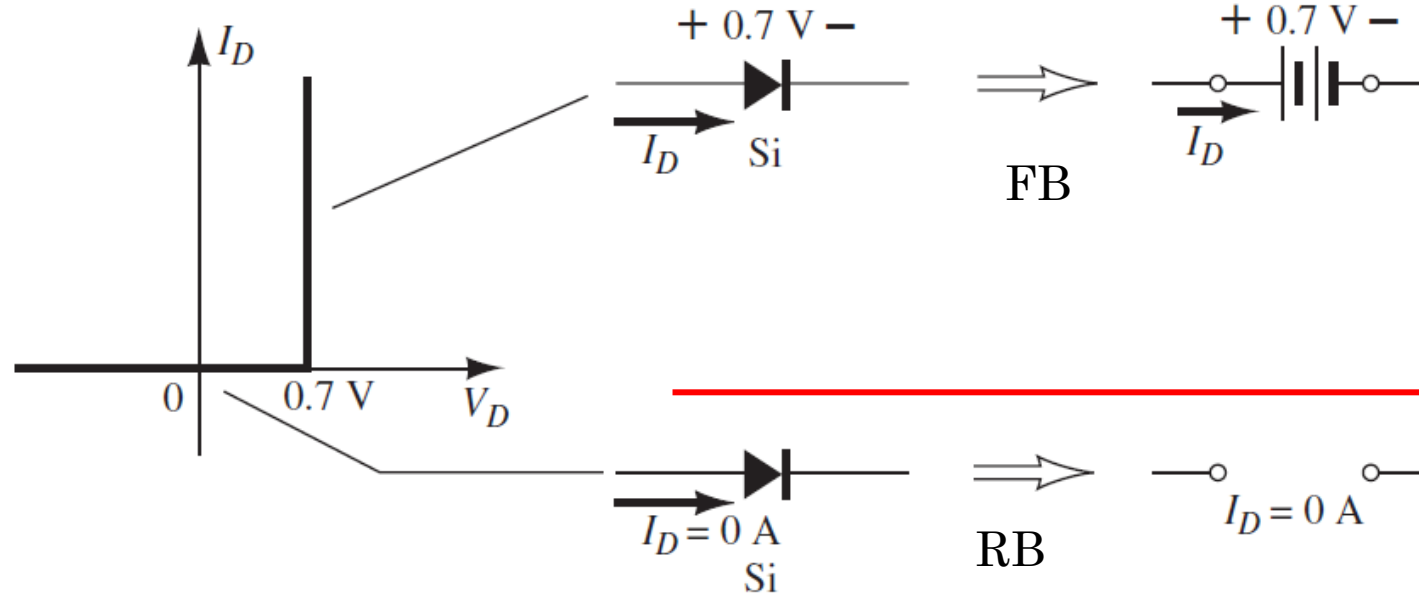


ON State (If current exists in loop by source) then replace with $V_d = \text{Forward bias}$

Special Case: (No bias)
If current (I) NOT exists by source in loop then replace $V_d = 0$ (short circuit) $\rightarrow$ No bias condition.

OFF State
(Open Circuit) = Reverse bias

- In general, a diode is in the “on” state if the current established by the applied sources is such that its direction matches that of the arrow in the diode symbol, and $V_D > 0.7$ V for silicon, $V_D > 0.3$ V for germanium, and $V_D > 1.2$ V for gallium arsenide.
- If no current exists in loop then $I = 0$ and $V = 0$, leads to diode short circuit.

CASE-1

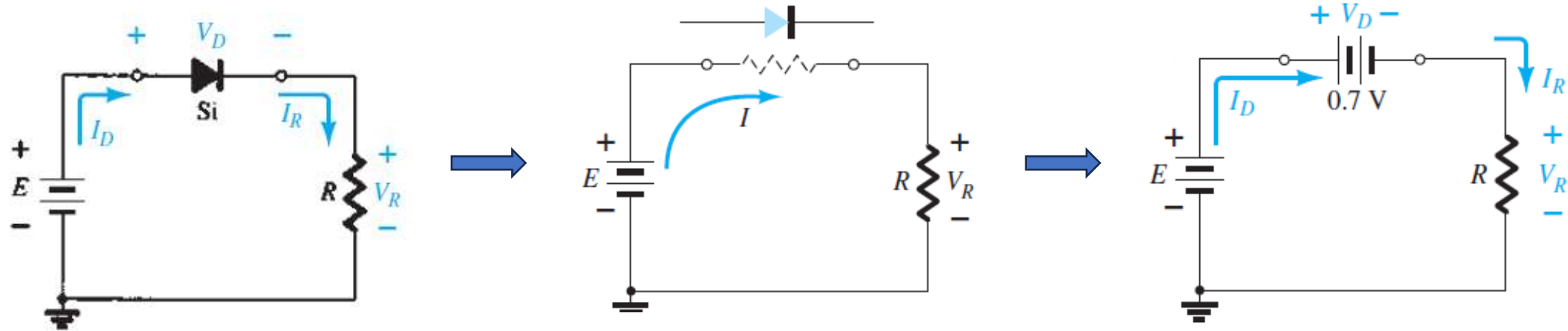


$$V_D = V_K$$

$$V_R = E - V_K$$

$$I_D = I_R = \frac{V_R}{R}$$

CASE-2

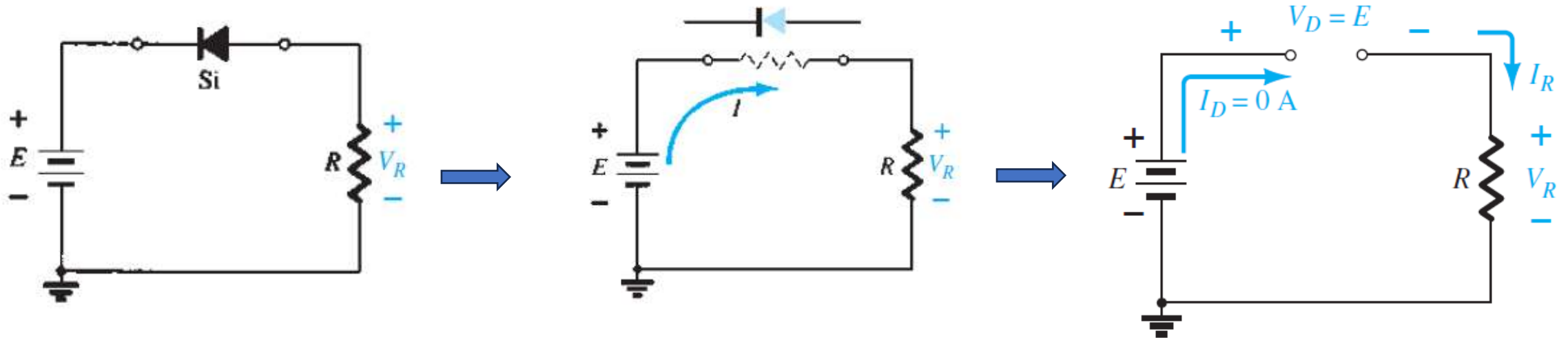

$$V_R = I_R R = I_D R = (0 \text{ A}) R = \mathbf{0 \text{ V}}$$

II).Problems on voltage across diode(Si /Ge) and Current through diode with DC source

1) For the series diode configuration of Fig below, determine V_D , V_R , and I_D .


- Since the applied voltage establishes a current in the clockwise direction to match the arrow of the symbol and the diode is in the “on” state,

$$V_D = 0.7 \text{ V}$$

$$V_R = E - V_D$$



$$= 8 \text{ V} - 0.7 \text{ V} = 7.3 \text{ V}$$
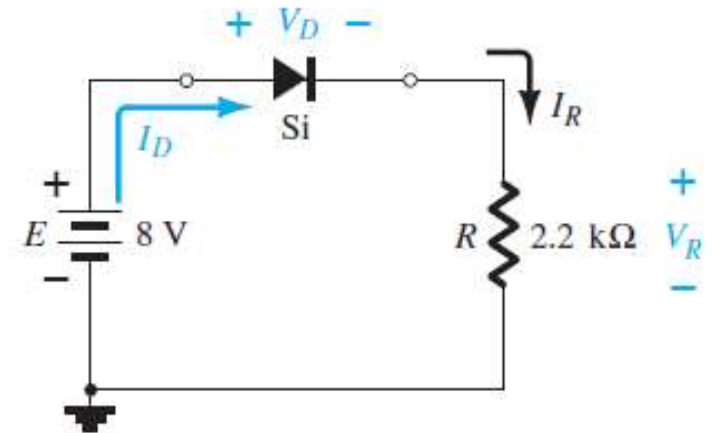
$$I_D = I_R = \frac{V_R}{R} = \frac{7.3 \text{ V}}{2.2 \text{ k}\Omega} \cong 3.32 \text{ mA}$$



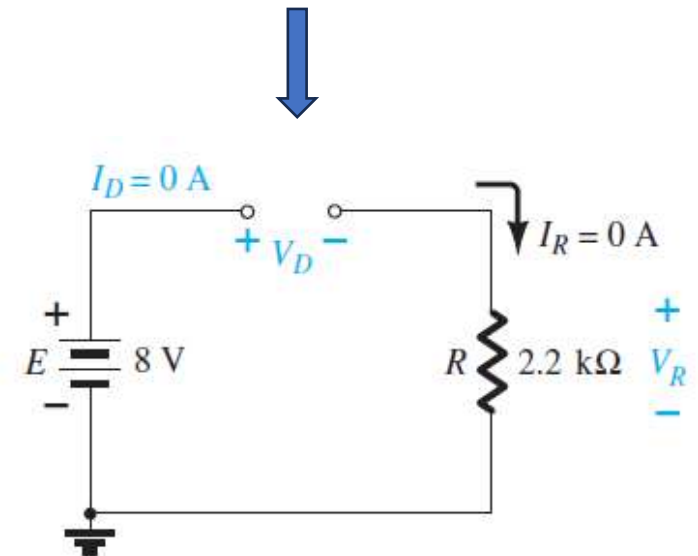
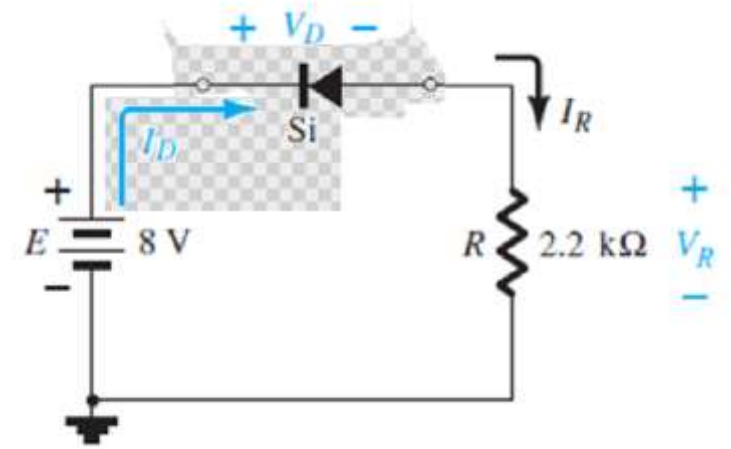
2) For the series diode configuration of Fig below, determine V_D , V_R , and I_D .

$$E - V_D - V_R = 0$$
$$V_D = E - V_R = E - 0 = E = 8 \text{ V}$$



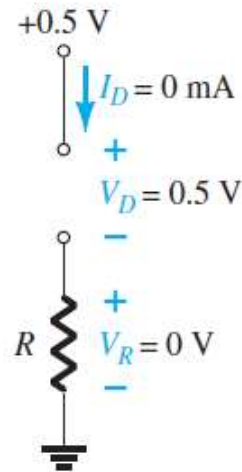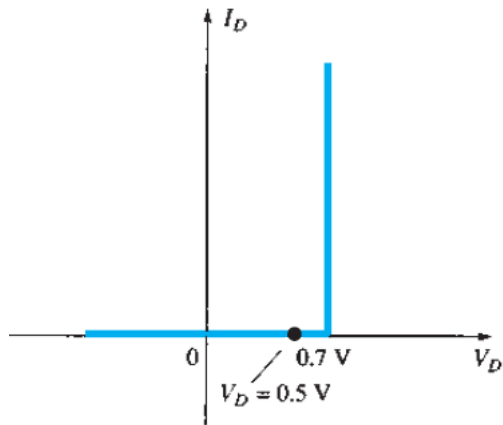3) For the series diode configuration of Fig below, determine V_D , V_R , and I_D .


- Although the “pressure” establishes a current with the same direction as the arrow symbol, the level of applied voltage is insufficient to turn the silicon diode “on.”




$$I_D = 0 \text{ A}$$

$$V_R = I_R R = I_D R = (0 \text{ A}) 1.2 \text{ k}\Omega = 0 \text{ V}$$

$$V_D = E = 0.5 \text{ V}$$

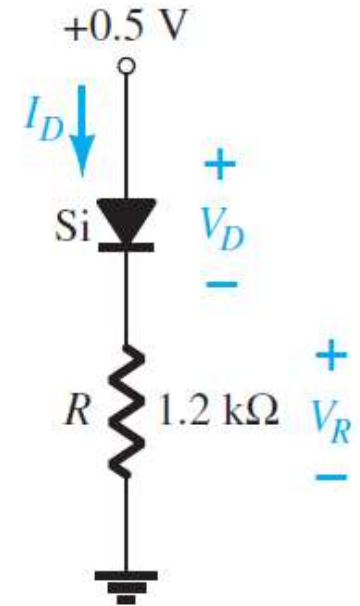

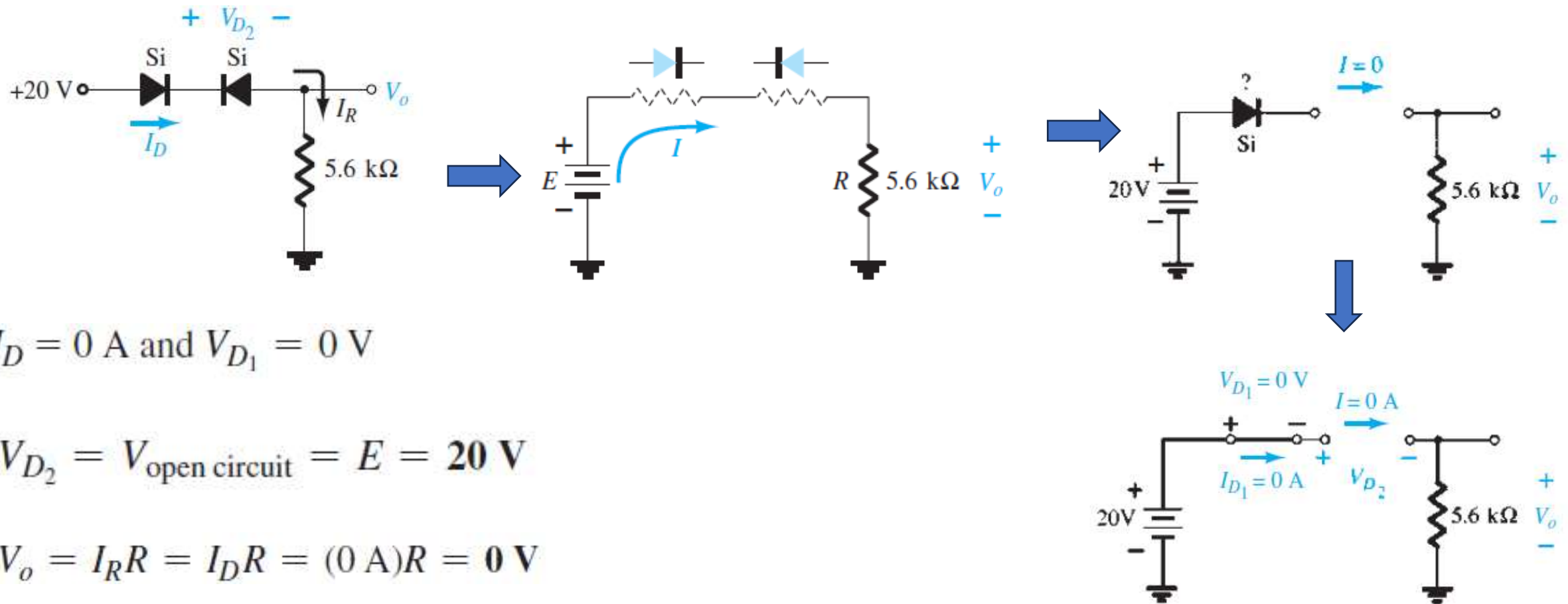4) Determine I_D , V_{D2} , and V_o for the circuit of Fig. below.




$$I_D = 0\text{ A and } V_{D1} = 0\text{ V}$$

$$V_{D2} = V_{\text{open circuit}} = E = 20\text{ V}$$

$$V_o = I_R R = I_D R = (0\text{ A})R = 0\text{ V}$$

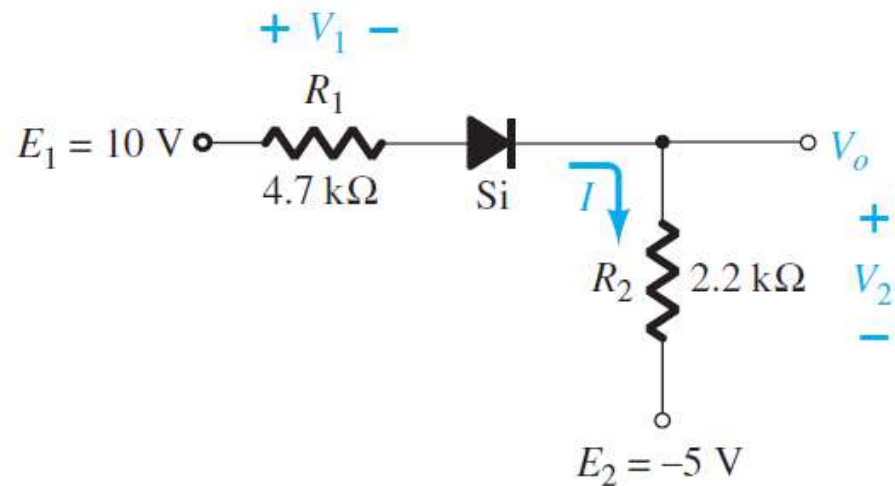5) Determine I , V_1 , V_2 , and V_o for the series dc configuration of Fig below.



$$I = \frac{E_1 + E_2 - V_D}{R_1 + R_2} = \frac{10\text{ V} + 5\text{ V} - 0.7\text{ V}}{4.7\text{ k}\Omega + 2.2\text{ k}\Omega} = \frac{14.3\text{ V}}{6.9\text{ k}\Omega} \cong 2.07\text{ mA}$$

$$V_1 = IR_1 = (2.07\text{ mA})(4.7\text{ k}\Omega) = 9.73\text{ V}$$

$$V_2 = IR_2 = (2.07\text{ mA})(2.2\text{ k}\Omega) = 4.55\text{ V}$$

$$-E_2 + V_2 - V_o = 0$$

$$V_o = V_2 - E_2 = 4.55\text{ V} - 5\text{ V} = -0.45\text{ V}$$

