



VIT-AP
UNIVERSITY

Fundamentals of Electrical and Electronics Engineering (FEEE)

SUB CODE: ECE1002

T-P-C: 3-2-4

Lecture-26

Faculty

Dr. Rajasekhar N V

Associate Professor G-1


SENSE, VIT-AP University

Mail: rajasekhar.venkata@vitap.ac.in


Cabin: Faculty Area 424-C:AB-1

Assignment Questions

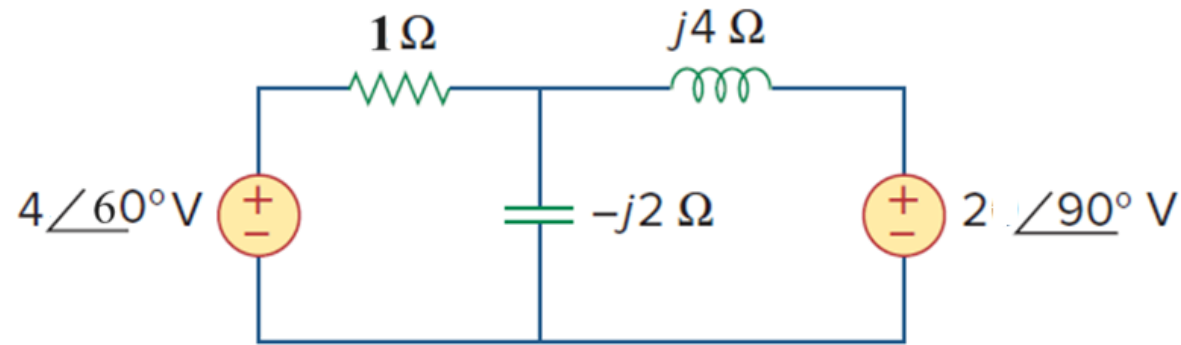
Calculate the average power of each element in the circuit of Fig. below.



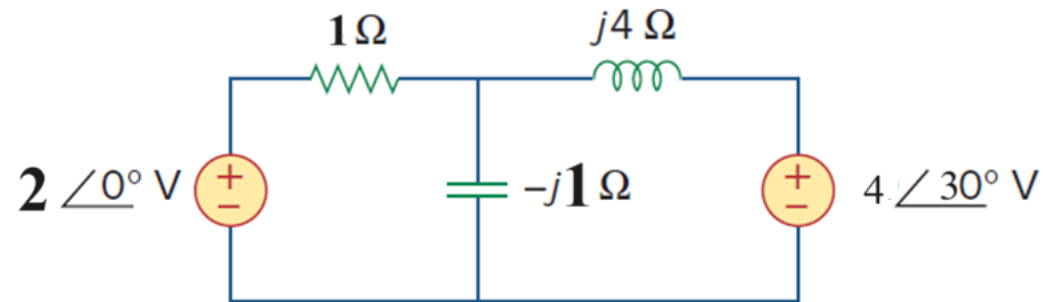Calculate the average power of the five elements in the circuit of Fig. below.



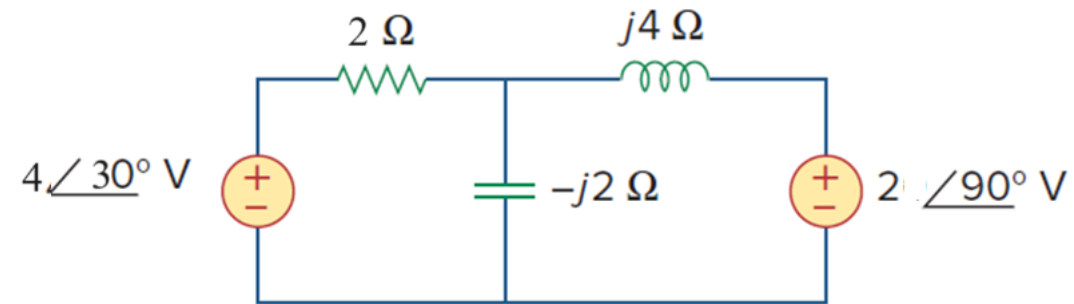Calculate the average power of the five elements in the circuit of Fig. below.



1) The following waveform is the voltage across a $15\text{-}\Omega$ resistor, calculate the average power absorbed by that resistor.

