



VIT-AP
UNIVERSITY

Fundamentals of Electrical and Electronics Engineering (FEEE)

SUB CODE: ECE1002

T-P-C: 3-2-4

Lecture-28

Faculty

Dr. Rajasekhar N V

Associate Professor G-1


SENSE, VIT-AP University

Mail: rajasekhar.venkata@vitap.ac.in


Cabin: Faculty Area 424-C:AB-1

Assignment Questions

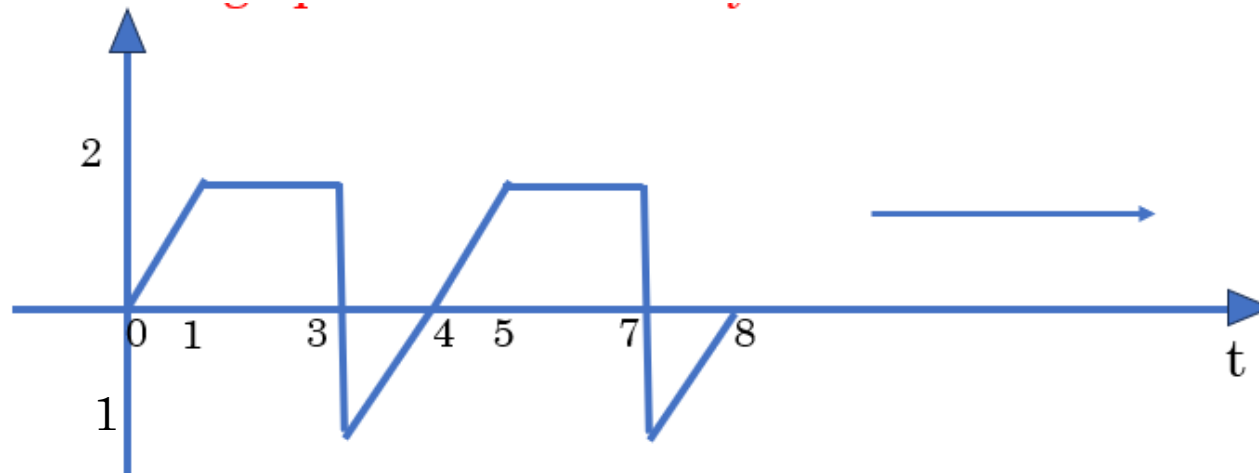
1) The following waveform is the voltage across a $15\text{-}\Omega$ resistor, calculate the average power absorbed by that resistor.



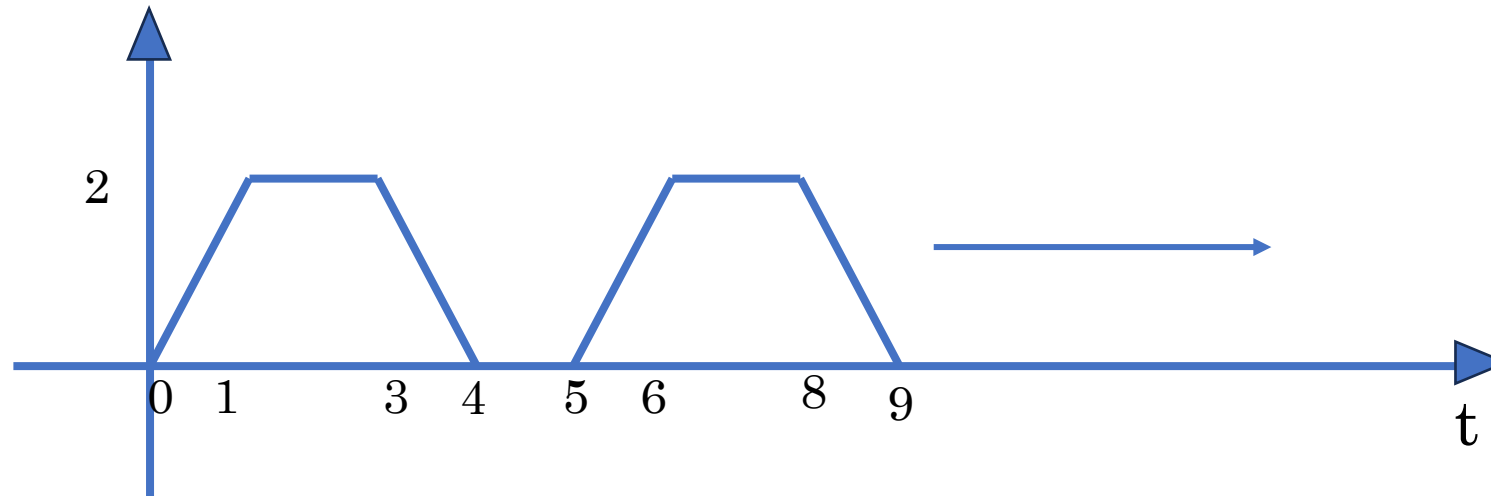- The following waveform is the voltage across a $10\text{-}\Omega$ resistor, calculate the average power absorbed by that resistor.



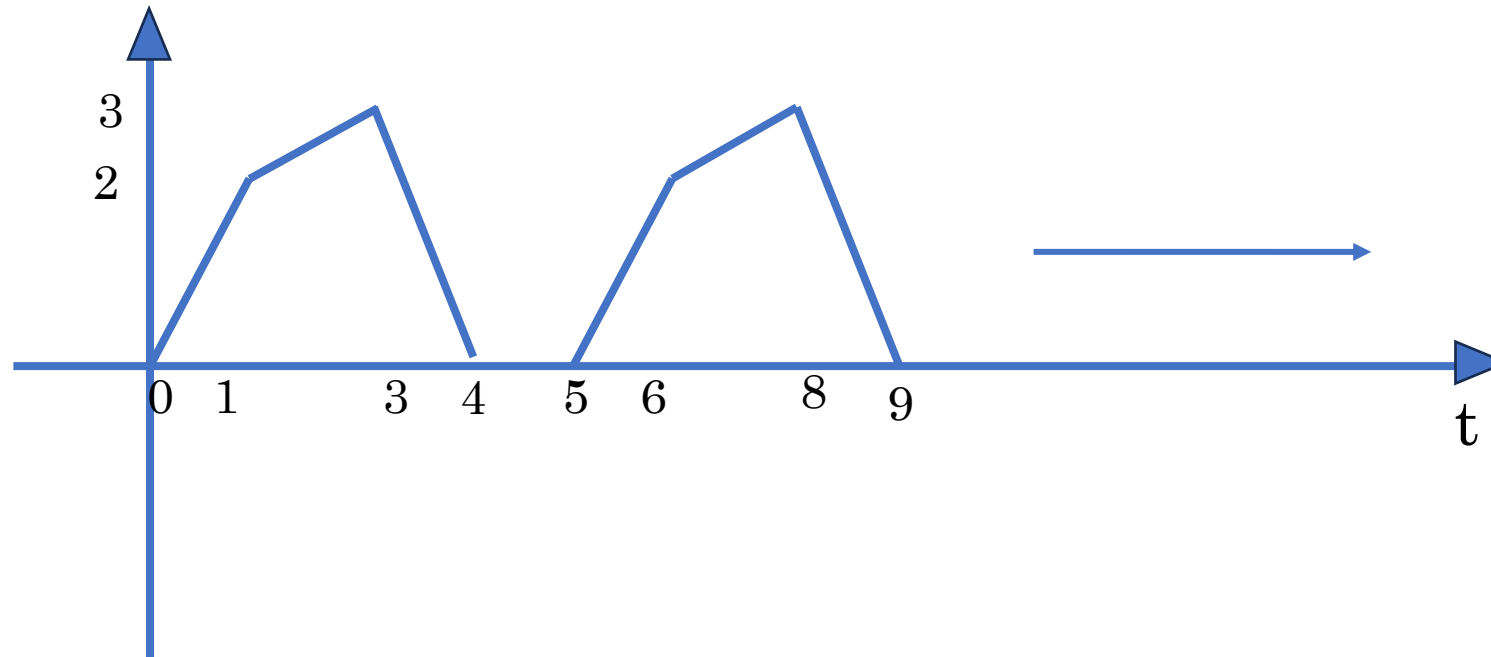- The following waveform is the voltage across a $5\text{-}\Omega$ resistor, calculate the average power absorbed by that resistor.



Determine I_{R1} , V_1 , V_{R2} , I_{R2} , V_{D2} , V_o and I_R for the circuit of Fig. below.

