



VIT-AP
UNIVERSITY

Fundamentals of Electrical and Electronics Engineering (FEEE)

SUB CODE: ECE1002

T-P-C: 3-2-4

Lecture-29

Faculty

Dr. Rajasekhar N V

Associate Professor G-1

SENSE, VIT-AP University

Mail: rajasekhar.venkata@vitap.ac.in

Cabin: Faculty Area 424-C:AB-1

Practice Questions

The voltage across a load is $v(t) = 10\sin(\omega t + 30^\circ)V$ and the current through the element in the direction of the voltage drop is $i(t) = 2\sin(\omega t + 60^\circ)A$. Find: (a) the complex and apparent powers, (b) the real and reactive powers, and (c) the power factor and the load impedance.

Find Z_{in} ?

$$10 \text{ mF} \Rightarrow \frac{1}{j\omega C} = \frac{1}{j4 \times 10 \times 10^{-3}} \\ = -j25 \Omega$$



$$5 \text{ H} \Rightarrow j\omega L = j4 \times 5 = j20 \Omega$$

Z_1 = Impedance of the 60- Ω resistor


Z_2 = Impedance of the parallel combination of the 10-mF capacitor and the 5-H inductor

Then $Z_1 = 60 \Omega$ and

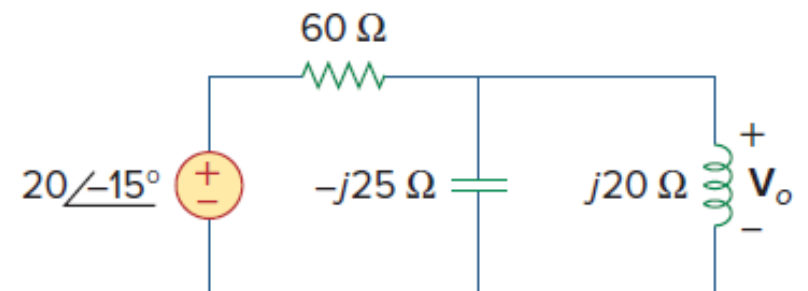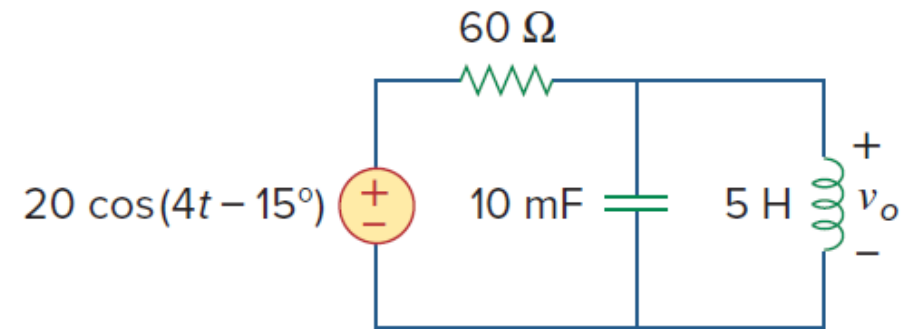
$$Z_2 = -j25 \parallel j20 = \frac{-j25 \times j20}{-j25 + j20} = j100 \Omega$$




Find Z_{in} ?

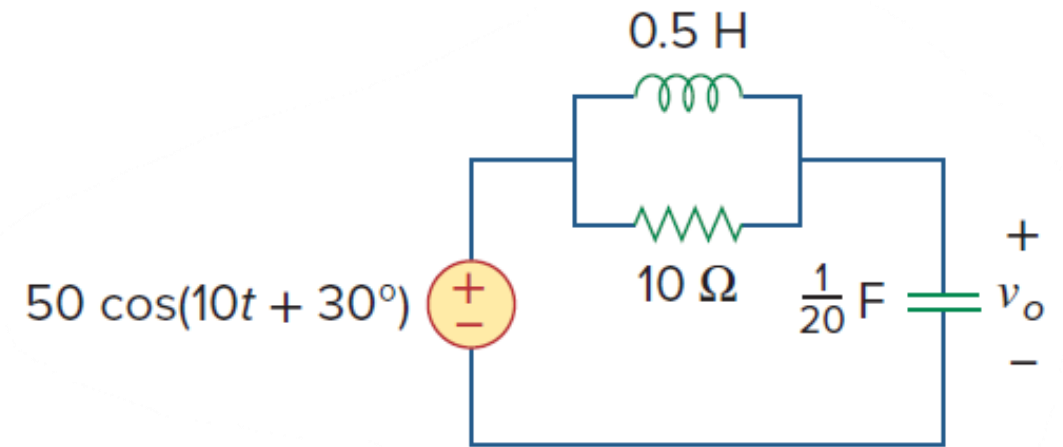

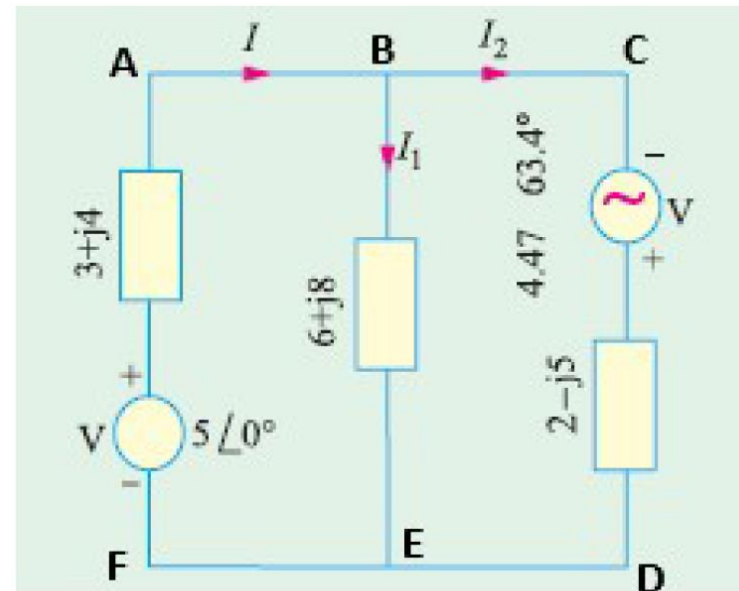
Using Kirchhoff's Laws, calculate the current flowing through each branch of the circuit shown in figure below.



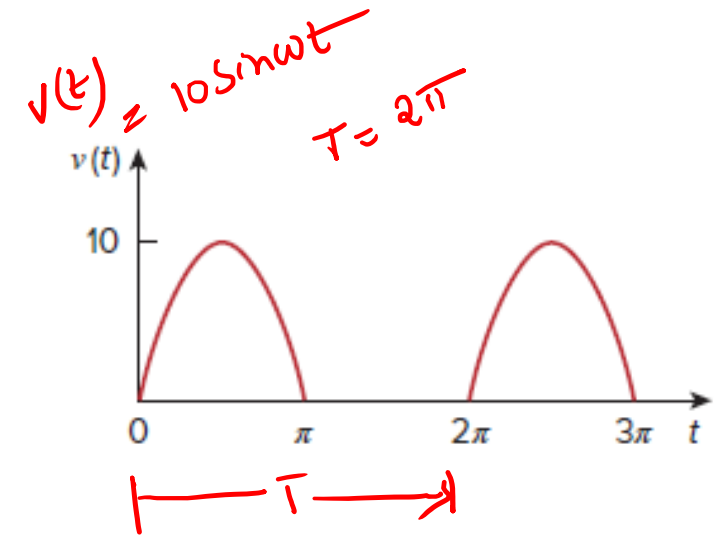The waveform shown in Fig. below is a half-wave rectified sine wave. Find the rms value and the amount of average power dissipated in a $10\text{-}\Omega$ resistor.



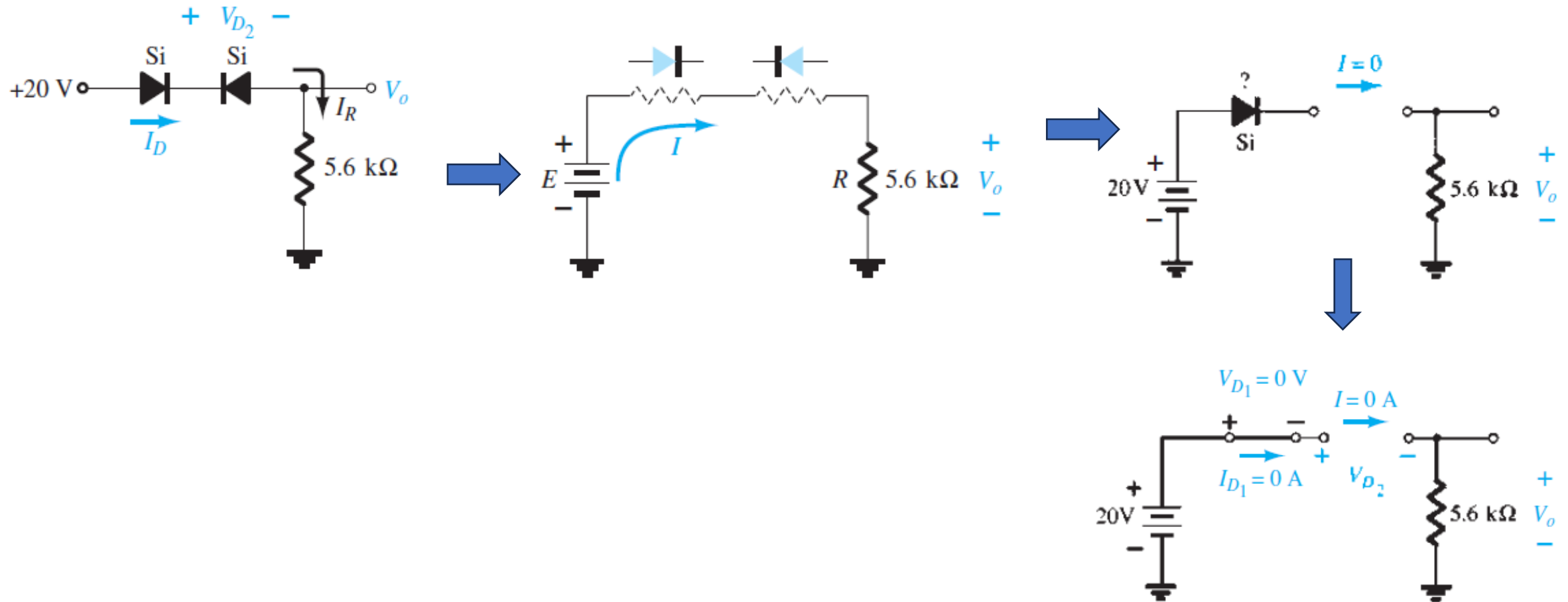Determine I_D , V_{D2} , and V_o for the circuit of Fig. below.



Determine I , V_1 , V_2 , and V_o for the series dc configuration of Fig below.

