

Fundamentals of Electrical and Electronics Engineering (FEEE)

SUB CODE: ECE1002

T-P-C: 3-2-4

Lecture-32

Faculty

Dr. Rajasekhar N V

Associate Professor G-1

SENSE, VIT-AP University

Mail: rajasekhar.venkata@vitap.ac.in

Cabin: Faculty Area 424-C:AB-1

Outline of Today's Class

- BJT Introduction
- BJT with fixed bias
- Problems

Bipolar Junction Transistor(BJT) Construction

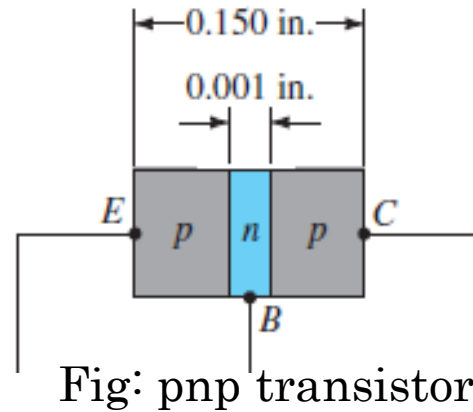


Fig: pnp transistor



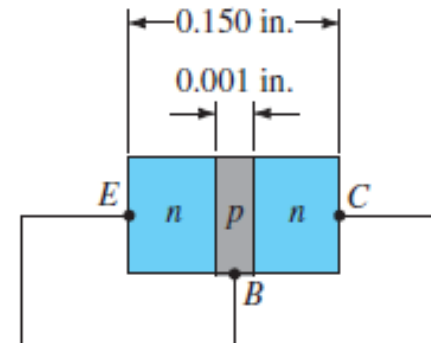


Fig: npn transistor

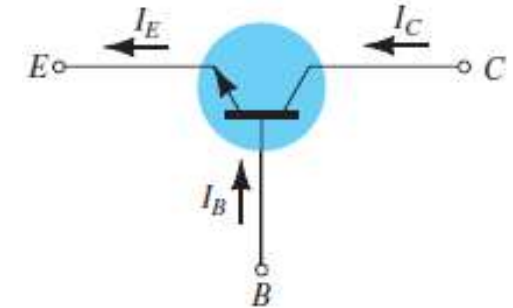

(a)

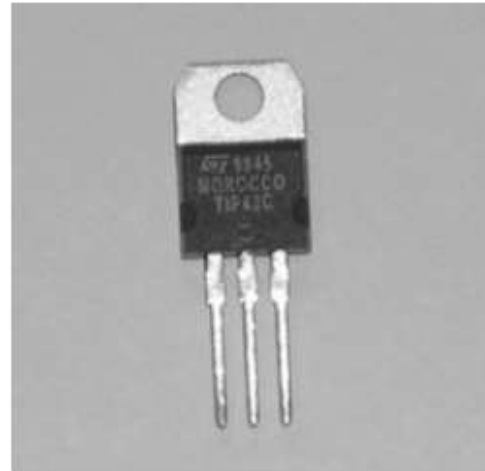

(b)



(c)

Various types of general-purpose or switching transistors: (a) low power; (b) medium power; (c) medium to high power.

Bipolar Junction Transistor(BJT) Construction

- The transistor is a three-layer semiconductor device consisting of either two n-type and one p-type layers of material or two p-type and one n-type layers of material.

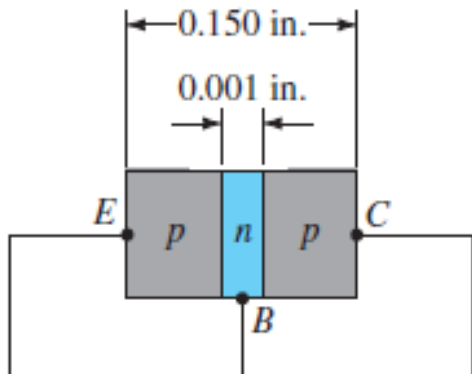


Fig: pnp transistor


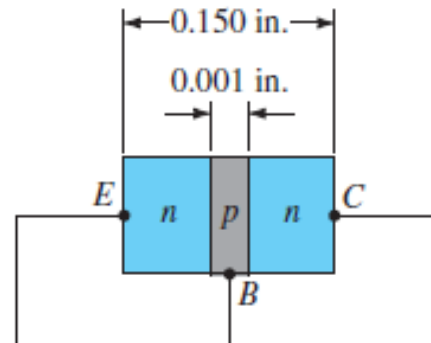
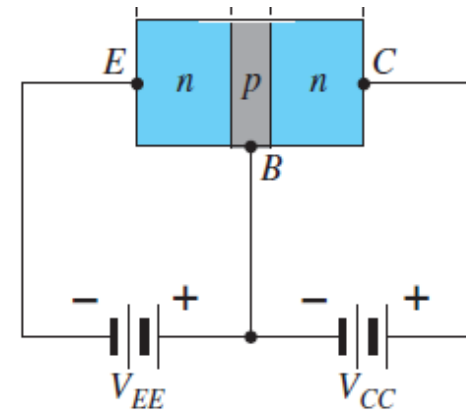


Fig: npn transistor

- E* for emitter ,
- C* for collector ,
- B* for base .


- The emitter layer is heavily doped, with the base and collector only lightly doped.
- The outer layers have widths much greater than the sandwiched *p* - or *n* -type material.

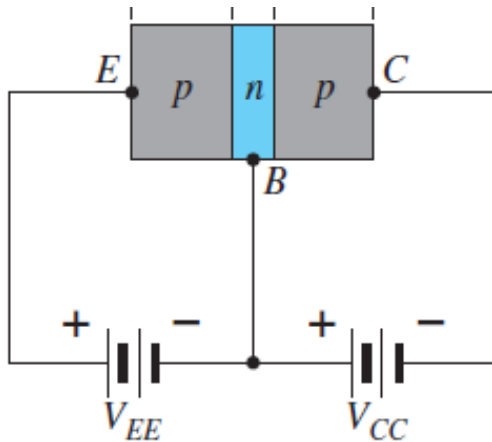- The abbreviation **BJT**, from **bipolar junction transistor**, is often applied to this three-terminal device. The term bipolar reflects the fact that holes and electrons participate in the injection process into the oppositely polarized material.
- If only one carrier is employed (electron or hole), it is considered a unipolar device.




Types of transistors: (a) pnp (b) npn.

Transistor Operation

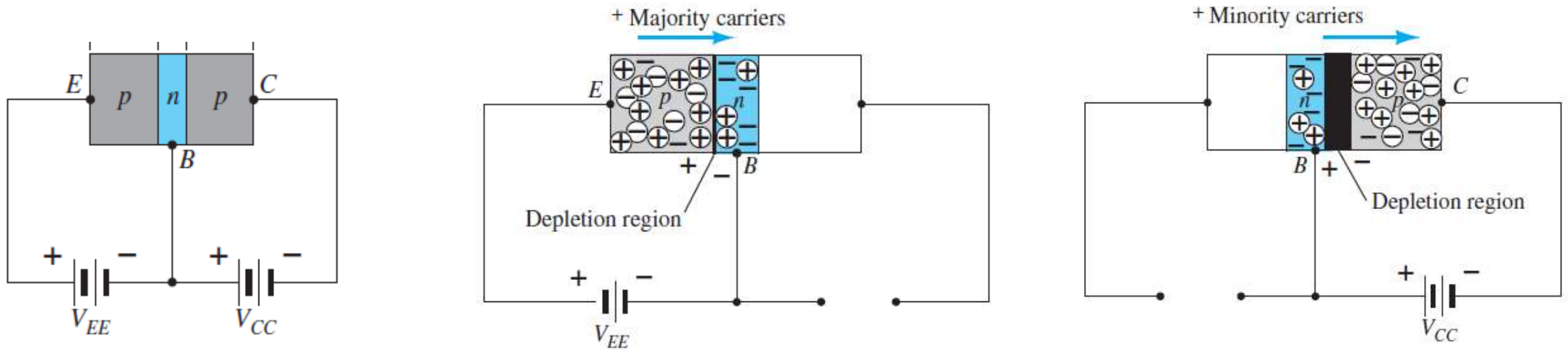


Biasing a transistor: (a) forward-bias;

(b) reverse-bias.


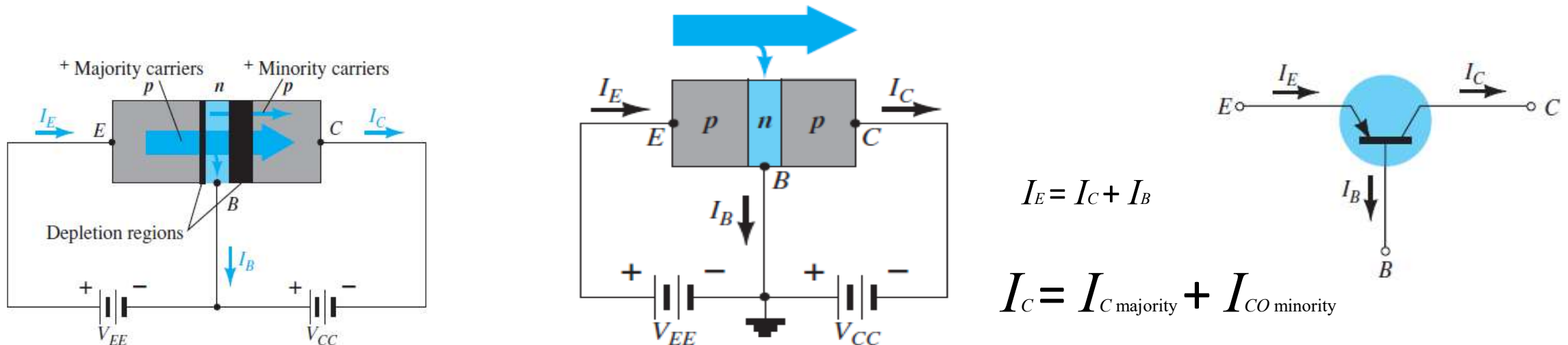




pnp

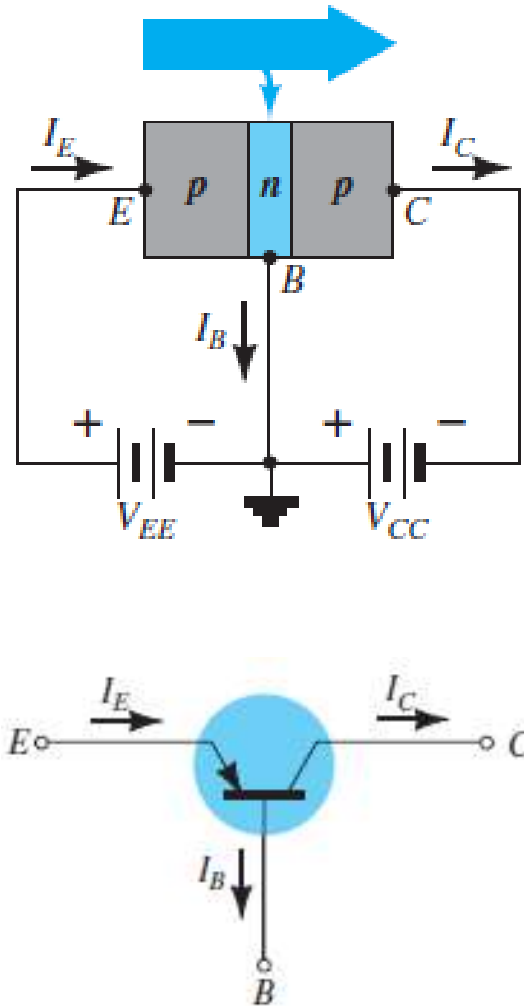


$$I_E = I_C + I_B$$

npn

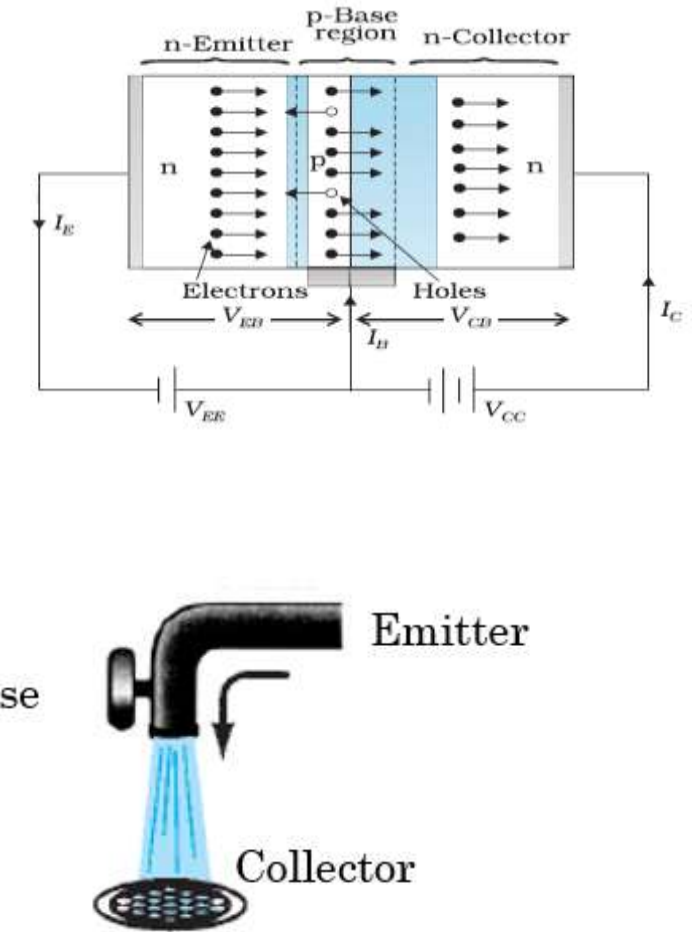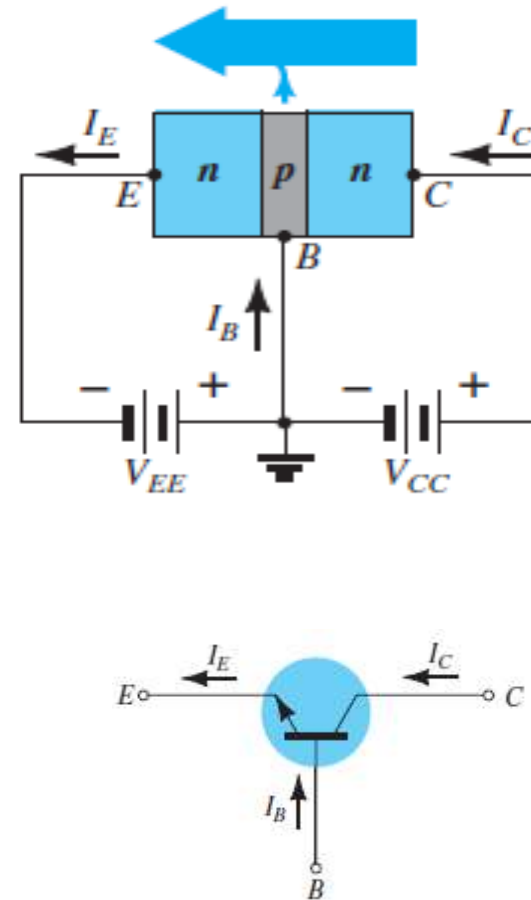

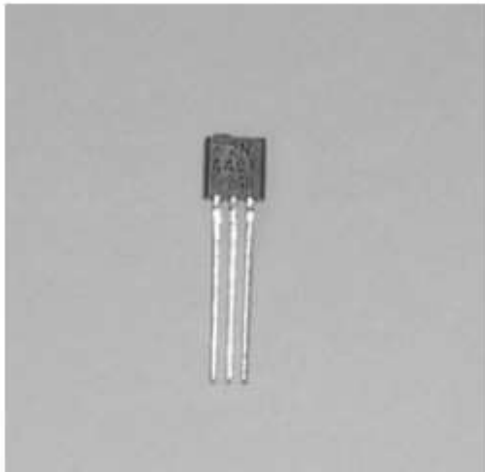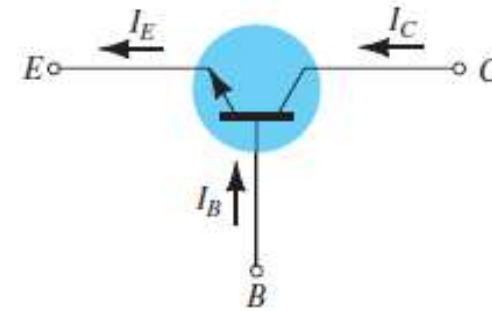

(a)

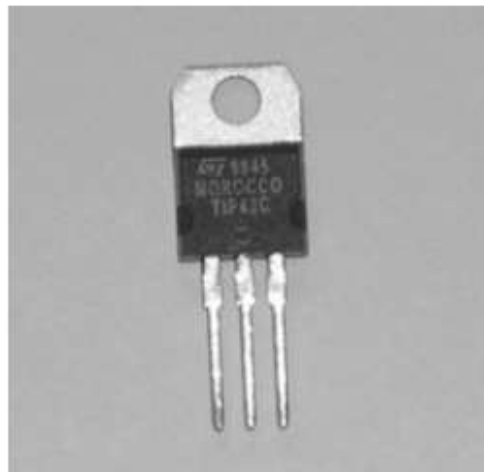

(b)





(c)

Various types of general-purpose or switching transistors: (a) low power; (b) medium power; (c) medium to high power.

BJT Configurations



1. Common-Base Configuration (CB)
2. Common-Emitter Configuration(CE)
3. Common-Collector Configuration(CC)

1.Common-Base(CB)

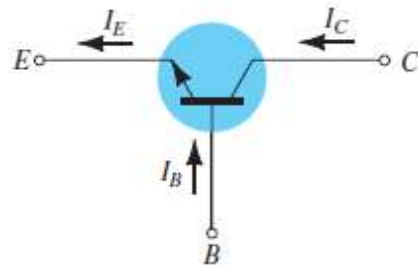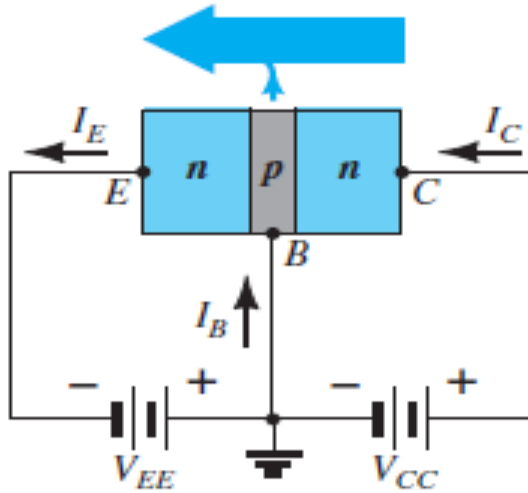

$$\alpha_{dc} = \frac{I_C}{I_E}$$



2.Common-Collector

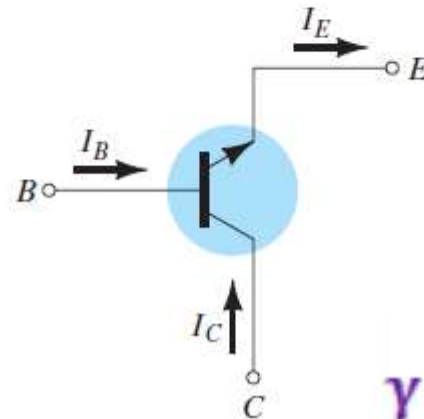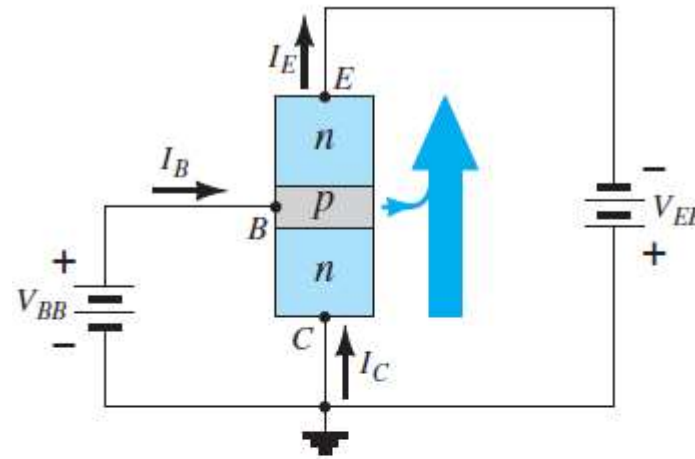

$$\gamma = \frac{\Delta I_E}{\Delta I_B}$$


$$I_E = I_C + I_B$$

3.Common-Emitter

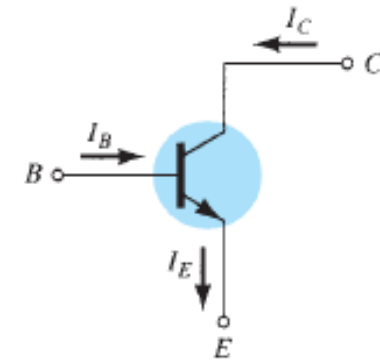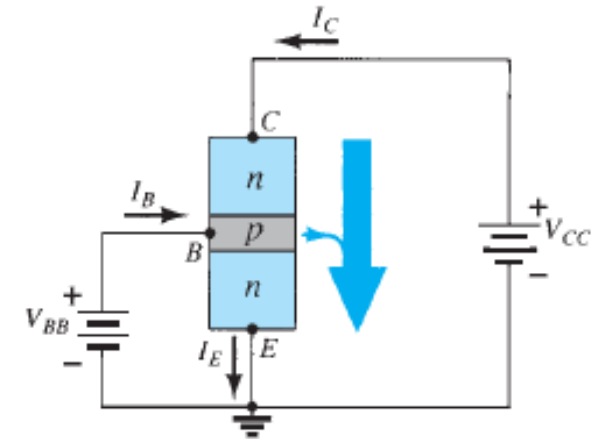


$$\beta_{dc} = \frac{I_C}{I_B}$$

1. Common-Base Configuration (CB)

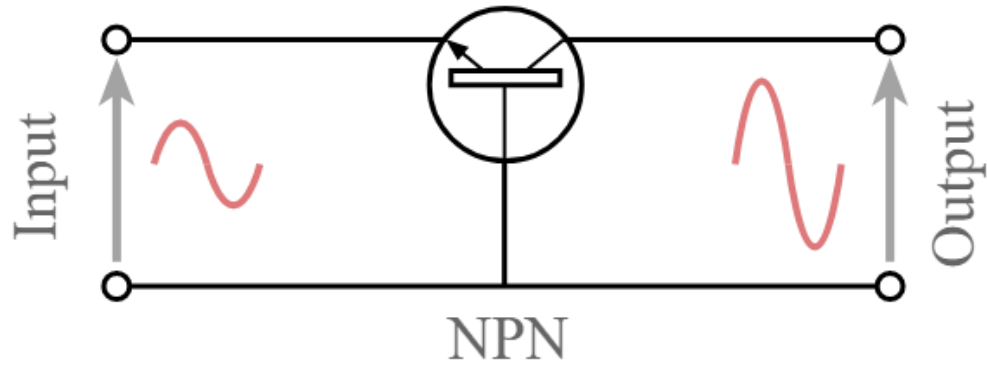


$$\alpha_{dc} = \frac{I_C}{I_E}$$

2. Common-Collector Configuration (CC)

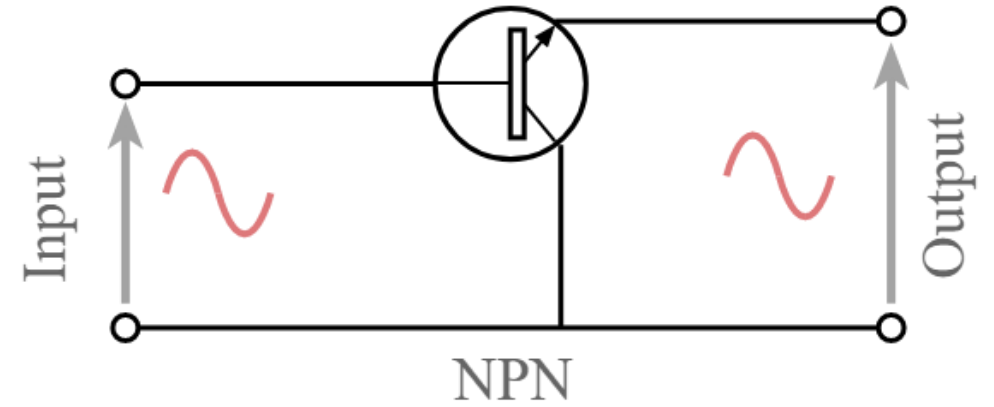



$$\gamma = \frac{I_E}{I_B}$$

3. Common-Emitter Configuration (CE)

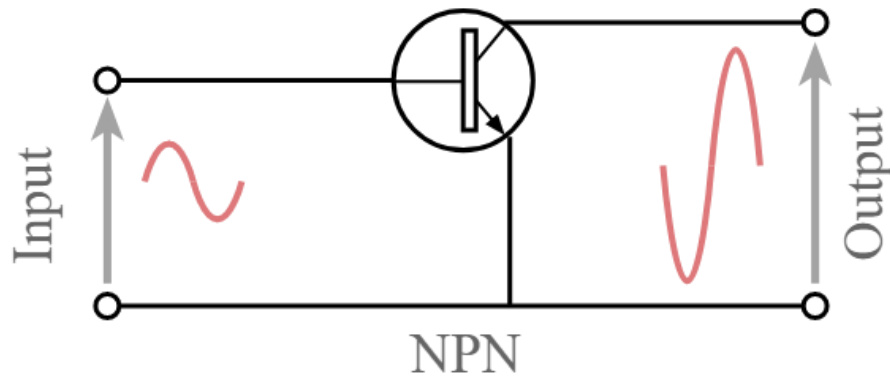

$$\beta_{dc} = \frac{I_C}{I_B}$$

3. Common-Emitter Configuration(CE)

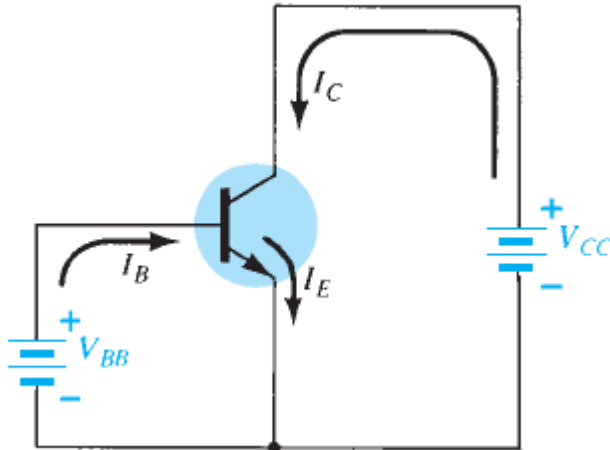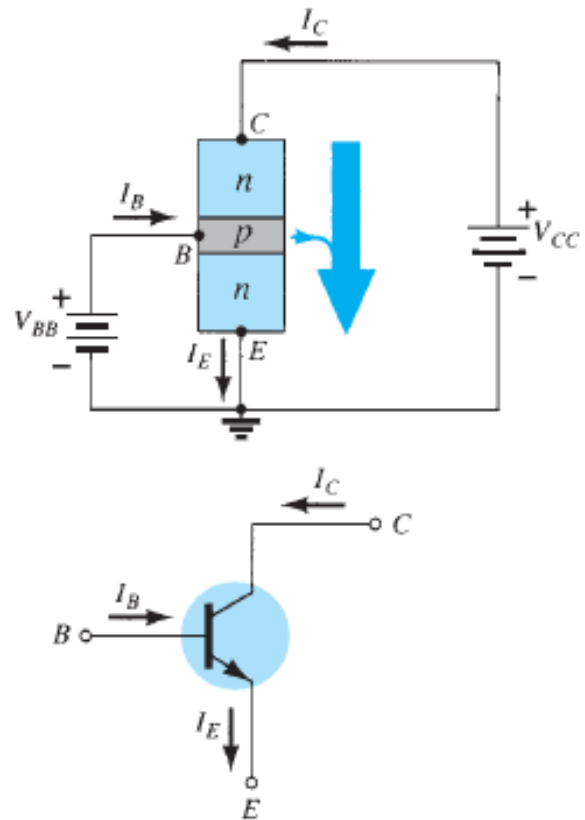

$$\beta_{dc} = \frac{I_C}{I_B}$$

$$I_C = \beta I_B$$

$$I_E = I_C + I_B$$
$$= \beta I_B + I_B$$

$$I_E = (\beta + 1)I_B \cong I_C$$