

Fundamentals of Electrical and Electronics Engineering (FEEE)

SUB CODE: ECE1002

T-P-C: 3-2-4

Lecture-36

Faculty

Dr. Rajasekhar N V


Associate Professor G-1

SENSE, VIT-AP University


Mail: rajasekhar.venkata@vitap.ac.in

Cabin: Faculty Area 424-C:AB-1

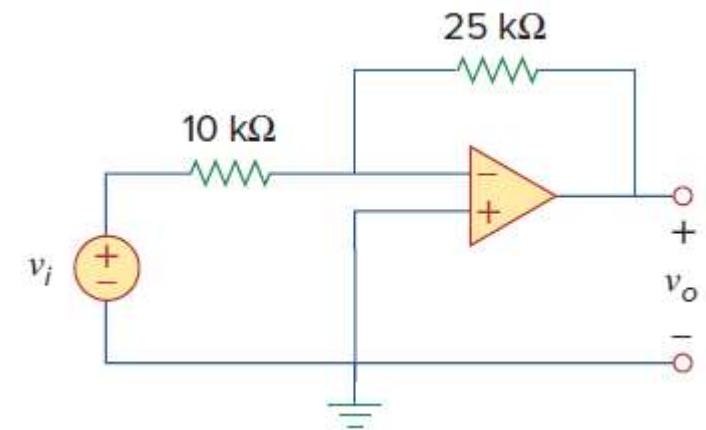1) Refer to the op amp in Fig. below. If $v_i = 0.5$ V, calculate: (a) the output voltage v_o , and (b) the current in the 10-k Ω resistor.



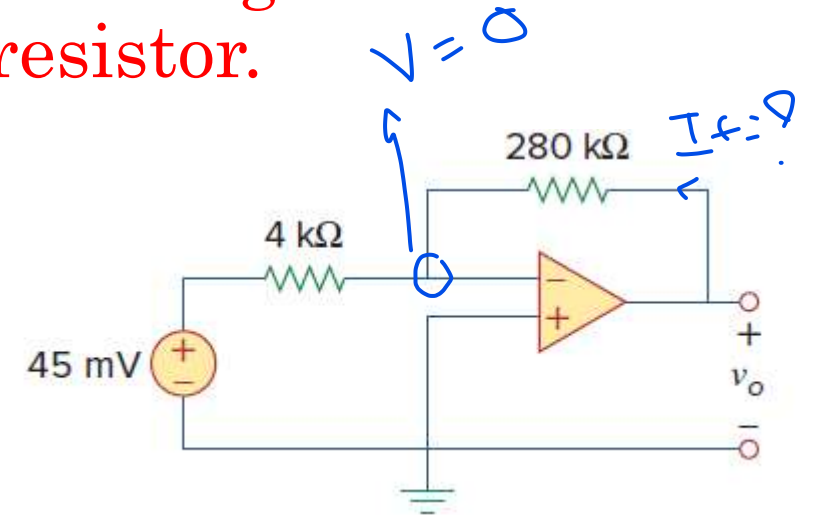2) Find the output of the op amp circuit shown in Fig. below.
Calculate the current through the feedback resistor.



$$V_o = \left(-\frac{R_f}{R_{in}} \right) V_{in}$$

$$= \left(-\frac{280}{4} \right) 45$$

$$= -3.15$$

$$I_f = \frac{3.15}{280} = 0.0011$$

- Q3) Design a circuit with one op-amp that provides a gain of 5.5. Assume you have a resistor $R_i = 10\text{k}\Omega$, what value would you choose for R_f ?

Q 4) Determine the input impedance and output voltage for the circuit in Figure

$$V_o = -\frac{20}{5} \times 100 = -400 \text{ mV}$$

