

Fundamentals of Electrical and Electronics Engineering (FEEE)

SUB CODE: ECE1002

T-P-C: 3-2-4

Lecture-37

Faculty

Dr. Rajasekhar N V


Associate Professor G-1

SENSE, VIT-AP University


Mail: rajasekhar.venkata@vitap.ac.in

Cabin: Faculty Area 424-C:AB-1

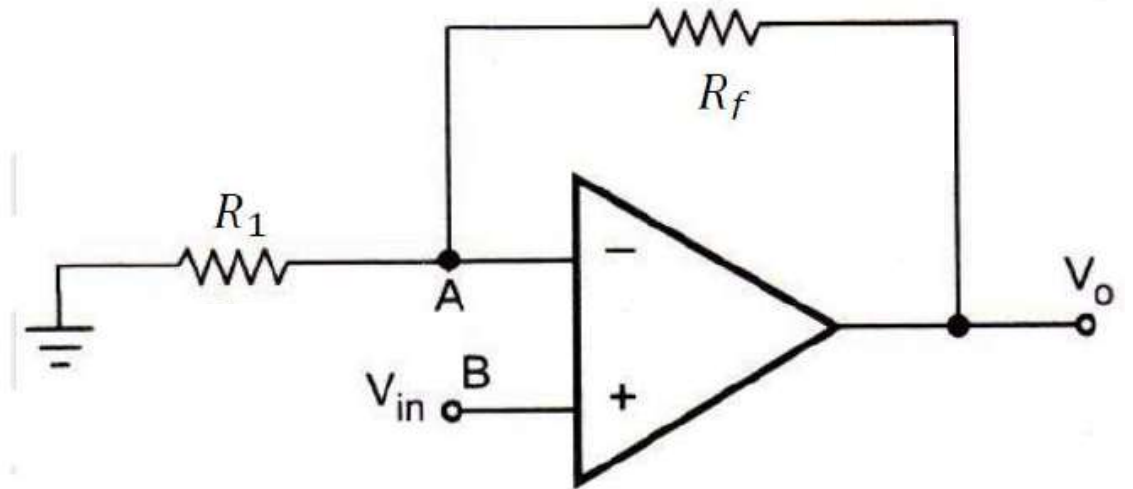5) If $V_{in}=5\text{ V}$ and ratio of R_f to R_1 is 2, then (a) find the output of the op amp circuit shown in Fig. below (b) Calculate the current through the feedback resistor if R_1 is $1\text{ k}\Omega$.



6. Find V_o in the following circuit.

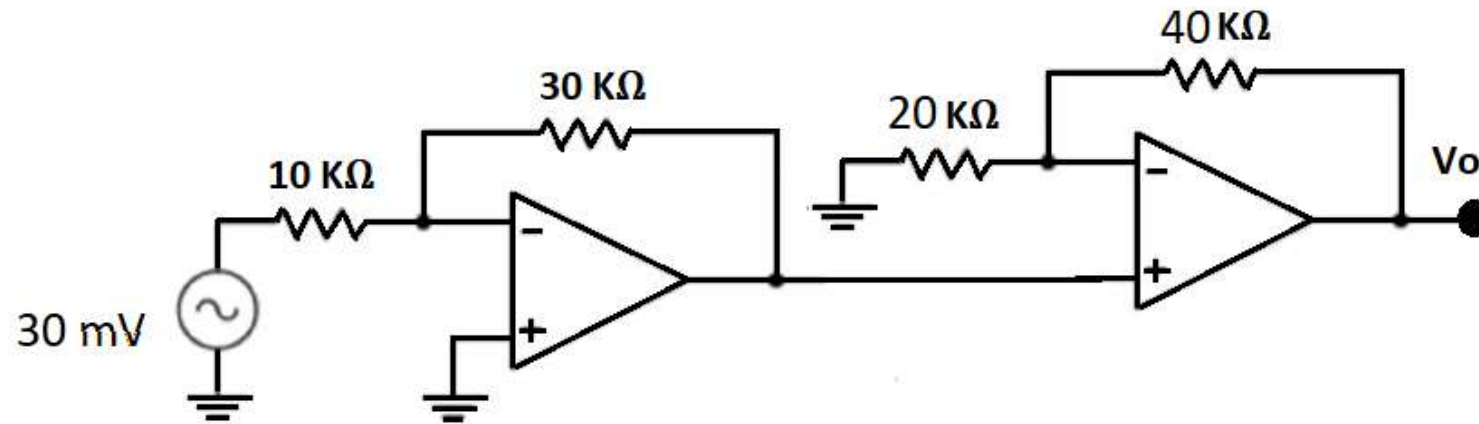

7. Find V_o in the following circuit.

