

**VIT-AP**  
**UNIVERSITY**

**DIGITAL LOGIC DESIGN**  
(Course Code: ECE 1003)

**Module-2:Lecture-8**

**Combinational Circuit Design**

# CONTENTS

## Module-2

- ❖ Binary adder and subtractor
- ❖ Ripple carry adders/subtractors and fast adders
- ❖ Binary decoders, encoders
- ❖ Multiplexers and de-multiplexers
- ❖ Logic functions using decoders and multiplexers
- ❖ Code converters
- ❖ **Magnitude comparator**

# CONTENTS

## Lecture-8

- ❖ Magnitude Comparator

# BOOKS

## Textbooks

1. M.Morris Mano, Michael D Ciletti, **Digital Design**, 5th edition, Pearson Publishers, 2013.
2. R.P. Jain, “**Modern Digital Electronics**”, 4th edition, TMH.

## References

1. M.Morris Mano, Charles R. Kime, Tom Martin, **Logic and Computer Design Fundamentals**, 4<sup>th</sup> edition, Pearson Publishers.
2. C. H. Roth and L. L. Kinney, **Fundamentals of Logic Design**, 5th edition, Cengage Publishers.

# Magnitude Comparator

## MAGNITUDE COMPARATOR

- ✓ A **magnitude digital Comparator** is a **combinational circuit** that compares two digital or binary numbers in order to find out whether one binary number is **equal, less than or greater than** the other binary number.
- ✓ We logically design a circuit for which we will have two inputs one for A and other for B and have three output terminals, one for  **$A > B$**  condition, one for  **$A = B$**  condition and one for  **$A < B$**  condition.



# MAGNITUDE COMPARATOR

## 1-bit Comparator

- ✓ A comparator used to compare two bits is called a **single bit comparator**.
- ✓ It consists of two inputs each for **two single bit numbers** and three outputs to generate **less than, equal to and greater than** between two binary numbers.
- ✓ From the truth table, the **Boolean expressions** can be obtained as

$$(A > B) = AB'$$

$$(A = B) = A'B' + AB$$

$$(A < B) = A'B$$

| A | B | A>B | A=B | A<B |
|---|---|-----|-----|-----|
| 0 | 0 | 0   | 1   | 0   |
| 0 | 1 | 0   | 0   | 1   |
| 1 | 0 | 1   | 0   | 0   |
| 1 | 1 | 0   | 1   | 0   |

# MAGNITUDE COMPARATOR


## 1-bit Comparator

- ✓ The circuit for 1 bit comparator circuit can be designed as

$$(A > B) = AB'$$

$$(A = B) = A'B' + AB$$

$$(A < B) = A'B$$

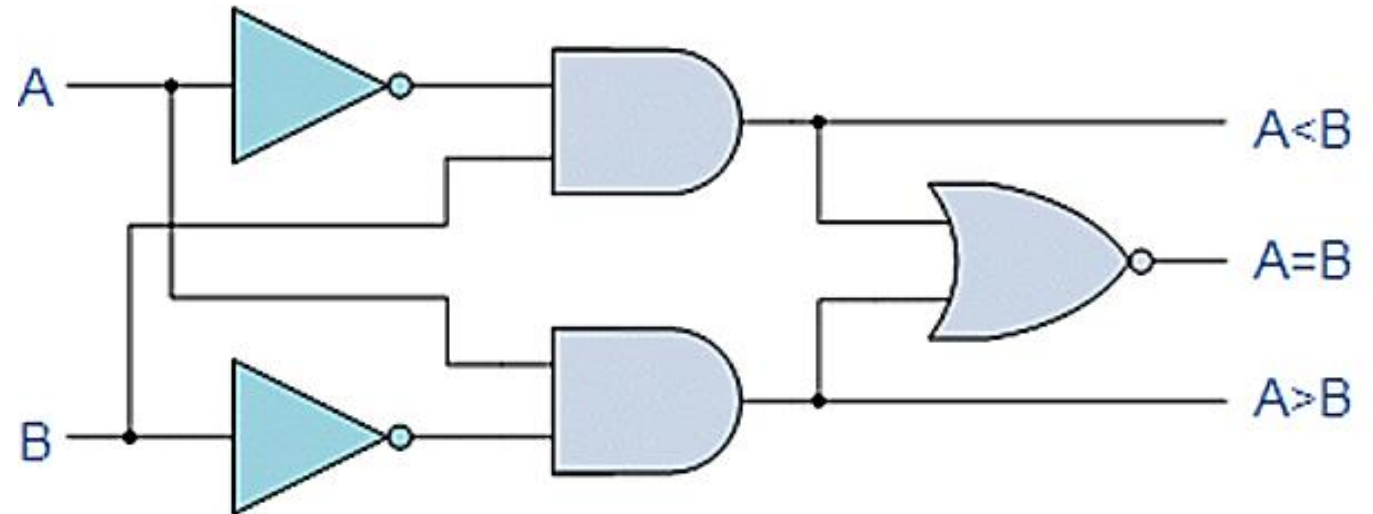



# MAGNITUDE COMPARATOR

## 2-bit Comparator


- ✓ A comparator used to compare **two binary numbers each of two bits** is called a **2-bit Magnitude comparator**.
- ✓ It consists of **four inputs and three outputs** to generate **less than, equal to and greater than** between two binary numbers.
- ✓ The truth table for a 2-bit comparator is given as:

| Inputs         |                |                |                | Outputs |     |     |
|----------------|----------------|----------------|----------------|---------|-----|-----|
| A <sub>1</sub> | A <sub>0</sub> | B <sub>1</sub> | B <sub>0</sub> | A>B     | A=B | A<B |
| 0              | 0              | 0              | 0              | 0       | 1   | 0   |
| 0              | 0              | 0              | 1              | 0       | 0   | 1   |
| 0              | 0              | 1              | 0              | 0       | 0   | 1   |
| 0              | 0              | 1              | 1              | 0       | 0   | 1   |
| 0              | 1              | 0              | 0              | 1       | 0   | 0   |
| 0              | 1              | 0              | 1              | 0       | 1   | 0   |
| 0              | 1              | 1              | 0              | 0       | 0   | 1   |
| 0              | 1              | 1              | 1              | 0       | 0   | 1   |
| 1              | 0              | 0              | 0              | 1       | 0   | 0   |
| 1              | 0              | 0              | 1              | 1       | 0   | 0   |
| 1              | 0              | 1              | 0              | 0       | 1   | 0   |
| 1              | 0              | 1              | 1              | 0       | 0   | 1   |
| 1              | 1              | 0              | 0              | 1       | 0   | 0   |
| 1              | 1              | 0              | 1              | 1       | 0   | 0   |
| 1              | 1              | 1              | 0              | 1       | 0   | 0   |
| 1              | 1              | 1              | 1              | 0       | 1   | 0   |

# MAGNITUDE COMPARATOR
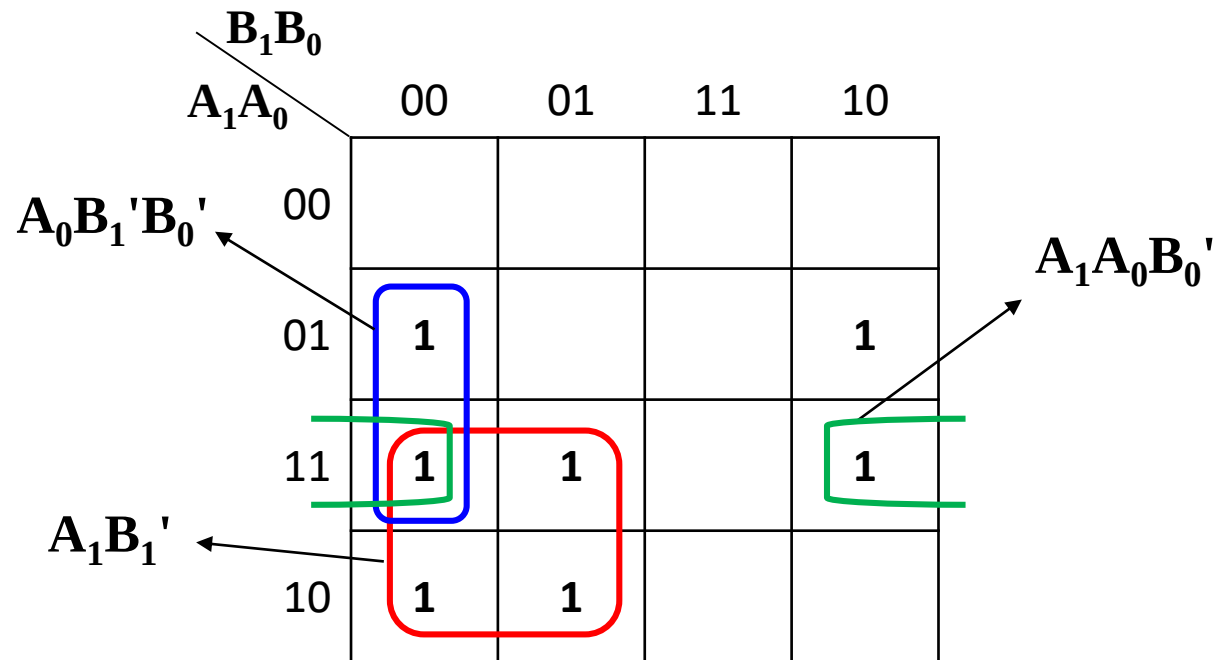
## 2-bit Comparator

- ✓ The Boolean functions for  $A > B$  can be obtained as



$$(A > B) = A_1B_1' + A_0B_1'B_0' + A_1A_0B_0'$$

# MAGNITUDE COMPARATOR

## 2-bit Comparator

- ✓ The Boolean functions for  $A=B$  can be obtained as


| $B_1B_0$<br>$A_1A_0 \backslash$ | 00 | 01 | 11 | 10 |
|---------------------------------|----|----|----|----|
| 00                              | 1  |    |    |    |
| 01                              |    | 1  |    |    |
| 11                              |    |    | 1  |    |
| 10                              |    |    |    | 1  |

$$\begin{aligned}(A = B) &= A_1'A_0'B_1'B_0' + A_1'A_0B_1'B_0 \\ &\quad + A_1A_0B_1B_0 + A_1A_0'B_1B_0' \\ &= A_1'B_1'(A_0'B_0' + A_0B_0) \\ &\quad + A_1B_1(A_0B_0 + A_0'B_0') \\ &= (A_0B_0 + A_0'B_0')(A_1B_1 + A_1'B_1') \\ &= (A_0 \odot B_0)(A_1 \odot B_1)\end{aligned}$$

# MAGNITUDE COMPARATOR
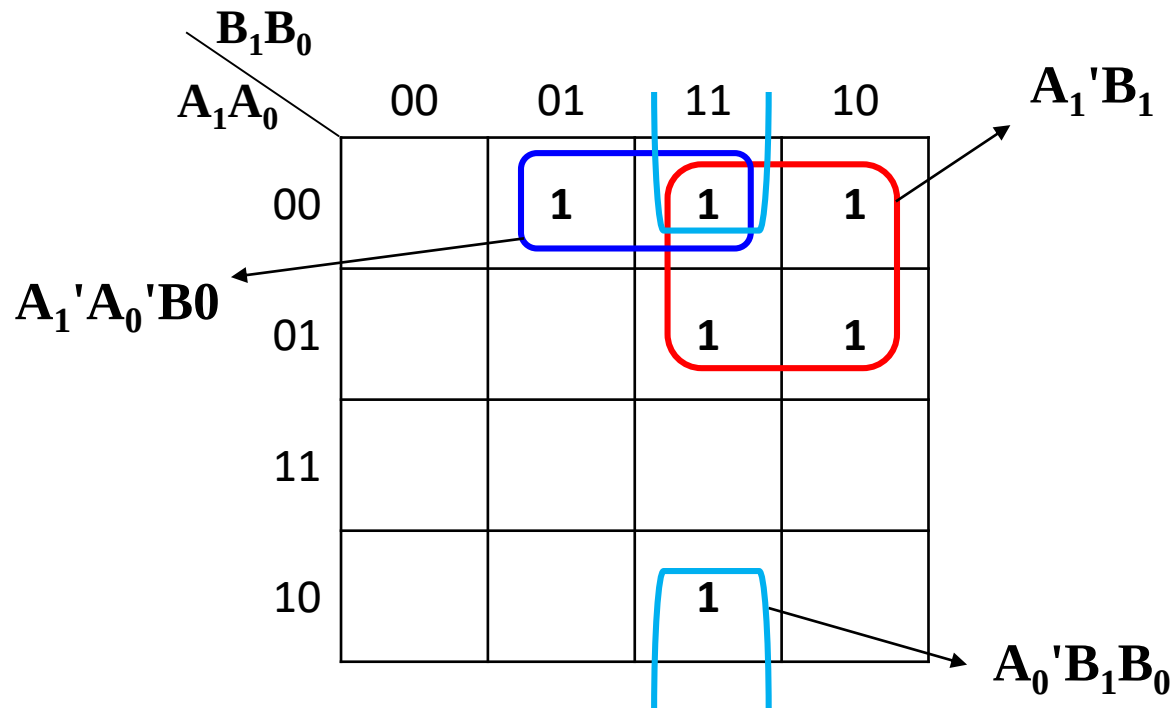
## 2-bit Comparator

- ✓ The Boolean functions for  $A < B$  can be obtained as




$$(A > B) = A_1'B_1 + A_0'B_1B_0 + A_1'A_0'B_0$$

# MAGNITUDE COMPARATOR
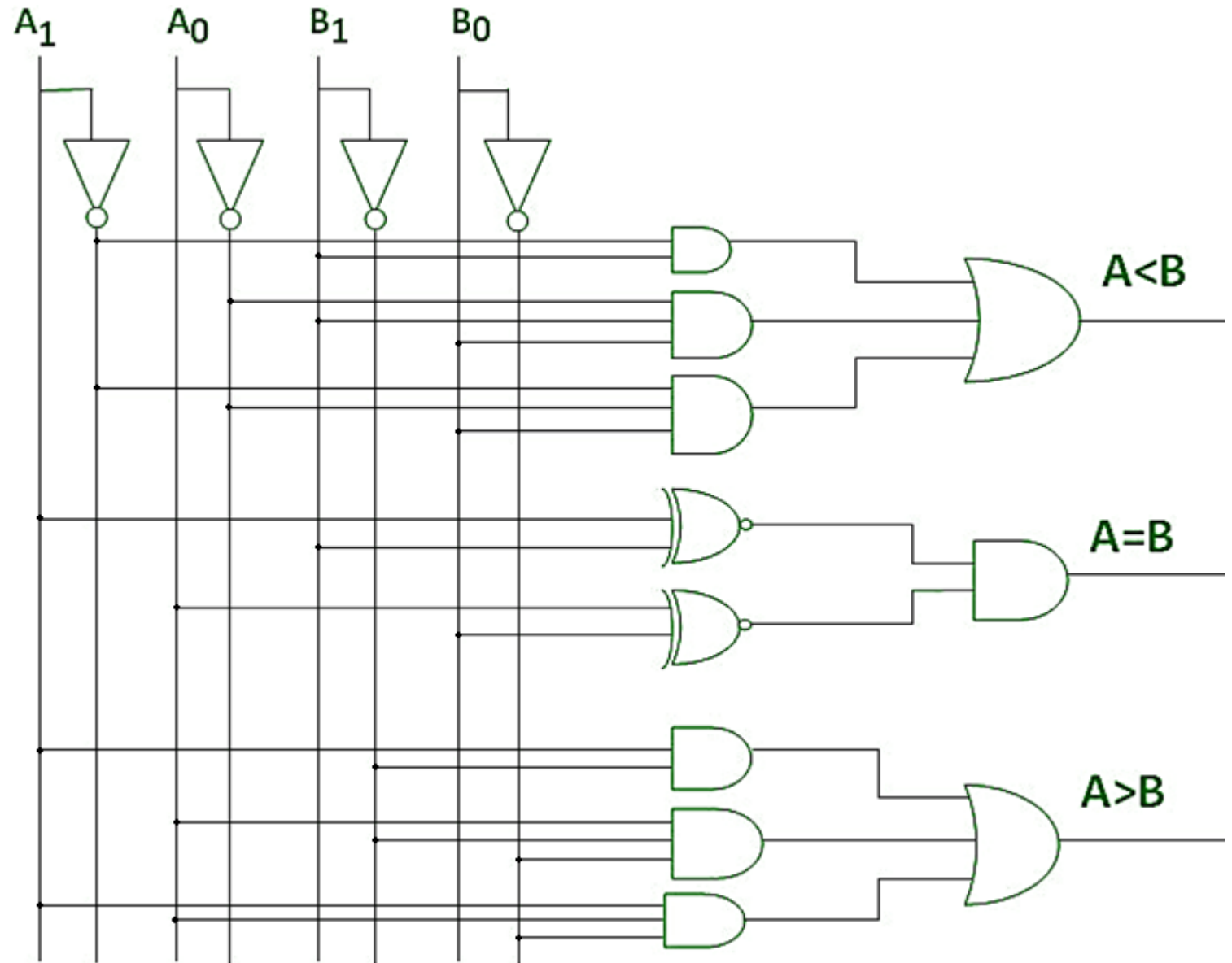
## 2-bit Comparator

- ✓ The Circuit for  $A < B$ ,  $A = B$  and  $A > B$  can be designed as



# MAGNITUDE COMPARATOR

## 4-bit Comparator

- ✓ A comparator used to compare **two binary numbers each of 4 bits** is called a **4-bit Magnitude comparator**.
- ✓ It consists of **eight inputs and three outputs** to generate **less than, equal to and greater than** between two binary numbers.
- ✓ In this case, the eight inputs will form  **$2^8 = 256$  possible input combinations** which is very difficult to analyze with truth table.
- ✓ Hence, a **direct Boolean function method** can be adopted in order to design the combinational circuit.
- ✓ Consider two numbers, A and B, with four digits each. Write the coefficients of the numbers in descending order of significance:

$$A = A_3 A_2 A_1 A_0$$

$$B = B_3 B_2 B_1 B_0$$

# MAGNITUDE COMPARATOR

## 4-bit Comparator

### 1. $A = B$ Condition:

- ✓ The two numbers are equal if all pairs of significant digits are equal:  $A_3 = B_3$ ,  $A_2 = B_2$ ,  $A_1 = B_1$ , and  $A_0 = B_0$ .
- ✓ When the numbers are binary, the digits are either 1 or 0, and the equality of each pair of bits can be expressed logically with an exclusive-NOR function as

$$x_i = A_i B_i + A'_i B'_i \quad \text{for } i = 0, 1, 2, 3$$

where  $x_i = 1$  only if the pair of bits in position  $i$  are equal (i.e., if both are 1 or both are 0).

- ✓ For equality to exist, all  $x_i$  variables must be equal to 1, a condition that dictates an AND operation of all variables:

$$(A = B) = x_3 x_2 x_1 x_0$$

The binary variable  $(A = B)$  is equal to 1 only if all pairs of digits of the two numbers are equal.

# MAGNITUDE COMPARATOR

## 4-bit Comparator

### 2. $A > B$ Condition:

- ✓ There are 4 possible cases through which we can analyze  $A > B$  condition

**Case-1:** If  $A_3 = 1$  and  $B_3 = 0$ , then  $A > B$

- ✓ We can write the Boolean expression as

$$(A > B) = A_3 B_3'$$

$$\begin{array}{rcl} \mathbf{A} & \rightarrow & \overset{A_3}{\textcircled{1}} \ 1 \ 0 \ 0 \\ \mathbf{B} & \rightarrow & \underset{B_3}{\textcircled{0}} \ 1 \ 0 \ 1 \end{array} \left. \vphantom{\begin{array}{rcl} \mathbf{A} & \rightarrow & \overset{A_3}{\textcircled{1}} \ 1 \ 0 \ 0 \\ \mathbf{B} & \rightarrow & \underset{B_3}{\textcircled{0}} \ 1 \ 0 \ 1 \end{array}} \right\} \mathbf{A} > \mathbf{B}$$

- ✓ The expression returns 1 if the above case occurred.



# MAGNITUDE COMPARATOR

## 4-bit Comparator

### 2. $A > B$ Condition:

**Case-2:** If  $A_3 = B_3$ ,  $A_2 = 1$  and  $B_2 = 0$ , then  $A > B$

- ✓ We can write the Boolean expression for  $A_3 = B_3$  as


$$(A=B) = A_3'B_3' + A_3B_3 = x_3$$

- ✓ Similarly, Boolean expression for  $A_2 = 1$  and  $B_2 = 0$  as

$$(A > B) = A_2B_2'$$

- ✓ The final expression can be obtained by performing the AND operation between both the conditions

$$(A > B) = x_3A_2B_2'$$

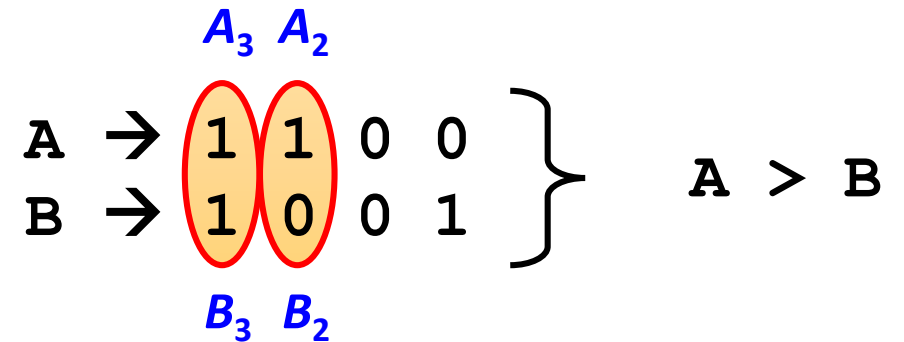

# MAGNITUDE COMPARATOR

## 4-bit Comparator

### 2. $A > B$ Condition:

**Case-3:** If  $A_3 = B_3$ ,  $A_2 = B_2$ ,  $A_1 = 1$  and  $B_1 = 0$ , then  $A > B$

- ✓ We can write the Boolean expression for  $A_3 = B_3$  and  $A_2 = B_2$  as


$$(A=B) = x_3x_2$$

- ✓ Similarly, Boolean expression for  $A_1 = 1$  and  $B_1 = 0$  as

$$(A > B) = A_1B_1'$$

- ✓ The final expression can be obtained by performing the AND operation between all the conditions

$$(A > B) = x_3x_2A_1B_1'$$

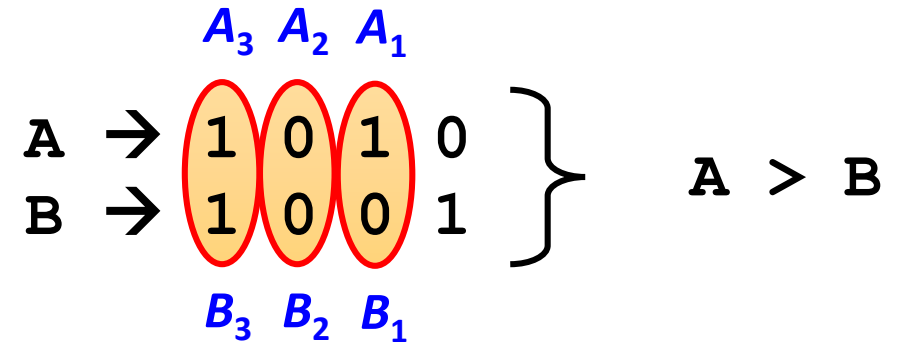

# MAGNITUDE COMPARATOR

## 4-bit Comparator

### 2. $A > B$ Condition:

**Case-4:** If  $A_3 = B_3$ ,  $A_2 = B_2$ ,  $A_1 = B_1$ ,  $A_0 = 1$  and  $B_0 = 0$ , then  $A > B$

- ✓ We can write the Boolean expression for  $A_3 = B_3$ ,  
 $A_2 = B_2$  and  $A_1 = B_1$  as


$$(A=B) = x_3x_2x_1$$

- ✓ Similarly, Boolean expression for  $A_0 = 1$  and  $B_0 = 0$  as

$$(A > B) = A_0B_0'$$

- ✓ The final expression can be obtained by performing the AND operation between all the conditions

$$(A > B) = x_3x_2x_1A_0B_0'$$

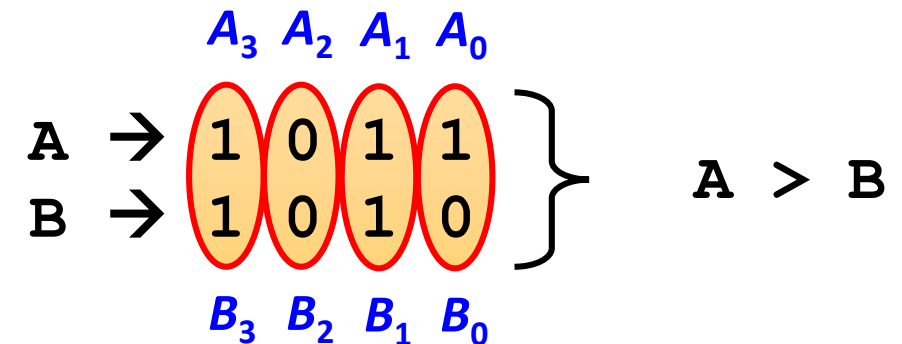

# MAGNITUDE COMPARATOR

## 4-bit Comparator

### 2. $A > B$ Condition:

- ✓ The final expression can be obtained by performing the AND operation between all the cases

$$(A > B) = A_3 B_3' + x_3 A_2 B_2' + x_3 x_2 A_1 B_1' + x_3 x_2 x_1 A_0 B_0'$$

### 3. $A < B$ Condition:


- ✓ Similarly, there are 4 possible cases through which we can analyze  $A < B$  condition.
- ✓ The final expression can be obtained by performing the AND operation between all the cases

$$(A < B) = A_3' B_3 + x_3 A_2' B_2 + x_3 x_2 A_1' B_1 + x_3 x_2 x_1 A_0' B_0$$

# MAGNITUDE COMPARATOR
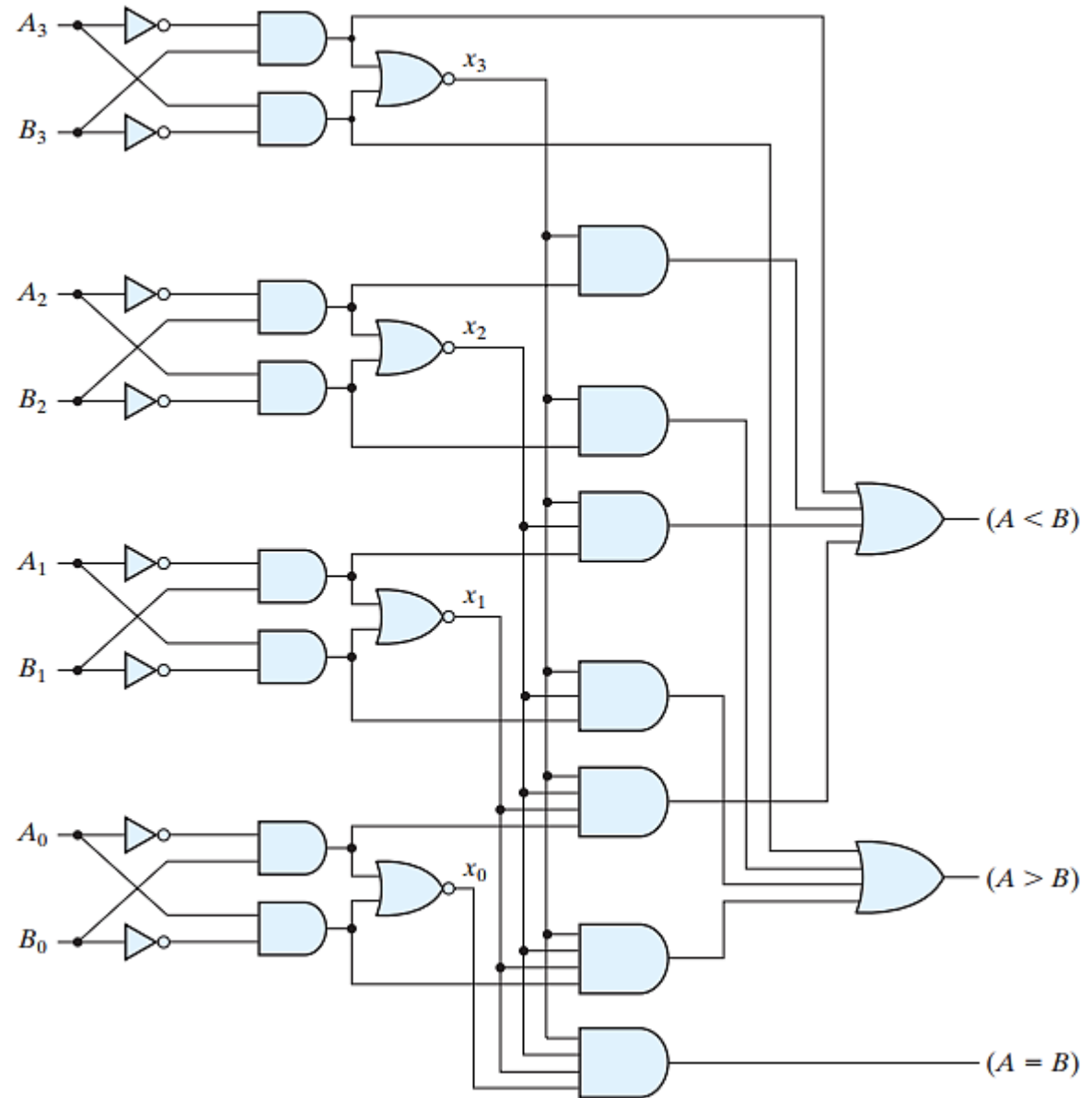
## 4-bit Comparator

- ✓ The Circuit for  $A < B$ ,  $A = B$  and  $A > B$  can be designed as



*Thank You*